

tangible

Digital Output

Tangible Matrix

Context	DIGITAL	ANALOG
INPUTS	BUTTON	POTENTIOMETER photoCell
OUTPUTS	LED BLINK	LED FADE

Digital OUTPUT

Context	DIGITAL	ANALOG
INPUTS	BUTTON	POTENTIOMETER photoCell
OUTPUTS	LED BLINK	LED FADE


REFERENCE

Digital Output

CONTEXT

	Digital	Analog
Input		
Output		

CIRCUIT

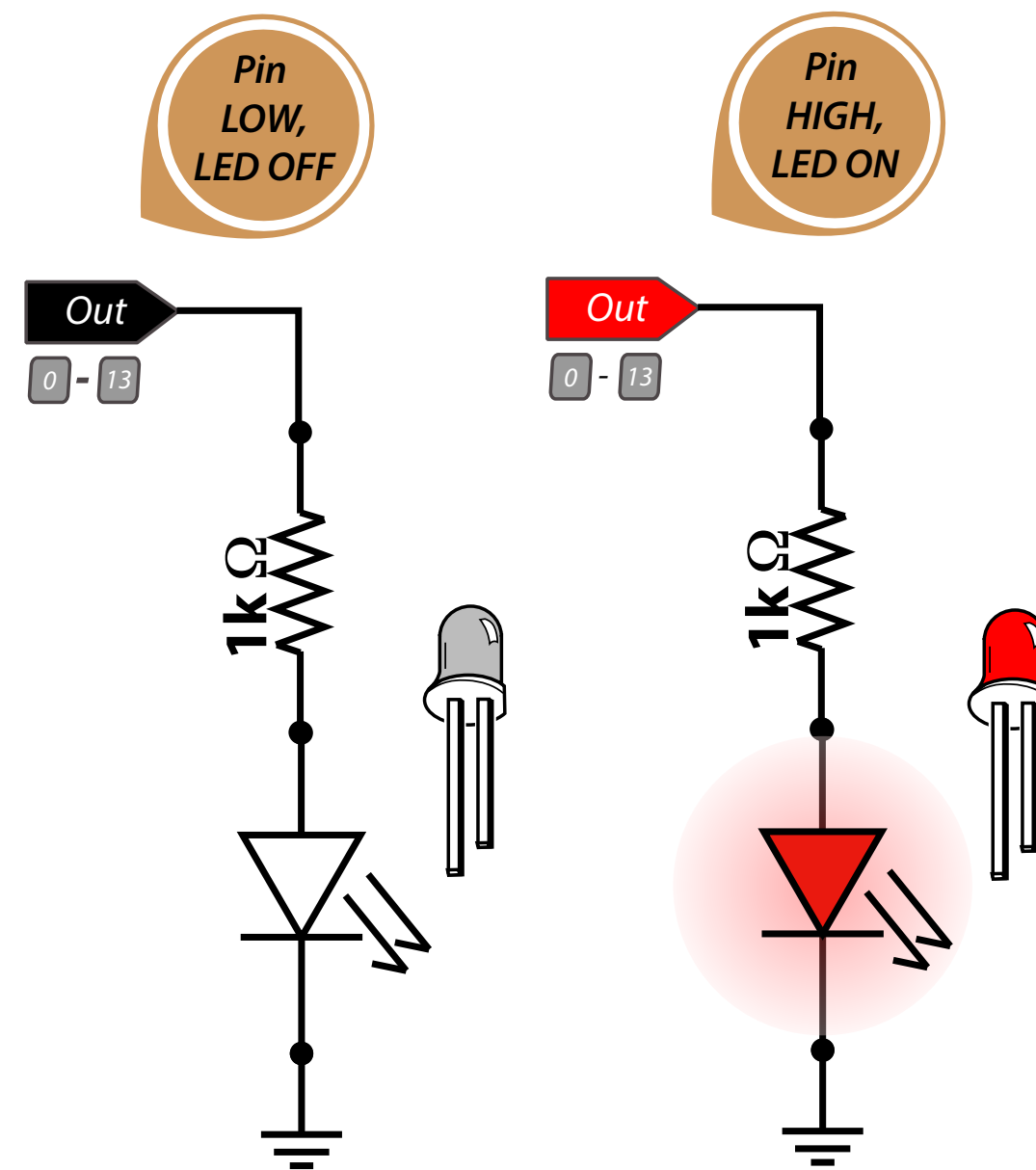

COMMAND

`digitalWrite ( pin, state );`
pin = 0-13
state = HIGH (1, 5V) , LOW (0, GND)

CODE

```
int ledPIN = 13;

void setup() {
    pinMode( ledPIN, OUTPUT );
}


void loop() {
    digitalWrite( ledPIN, 1 );
    delay(1000);

    digitalWrite( ledPIN, 0 );
    delay(1000);
}
```

The CONTEXT

INPUT / OUTPUT

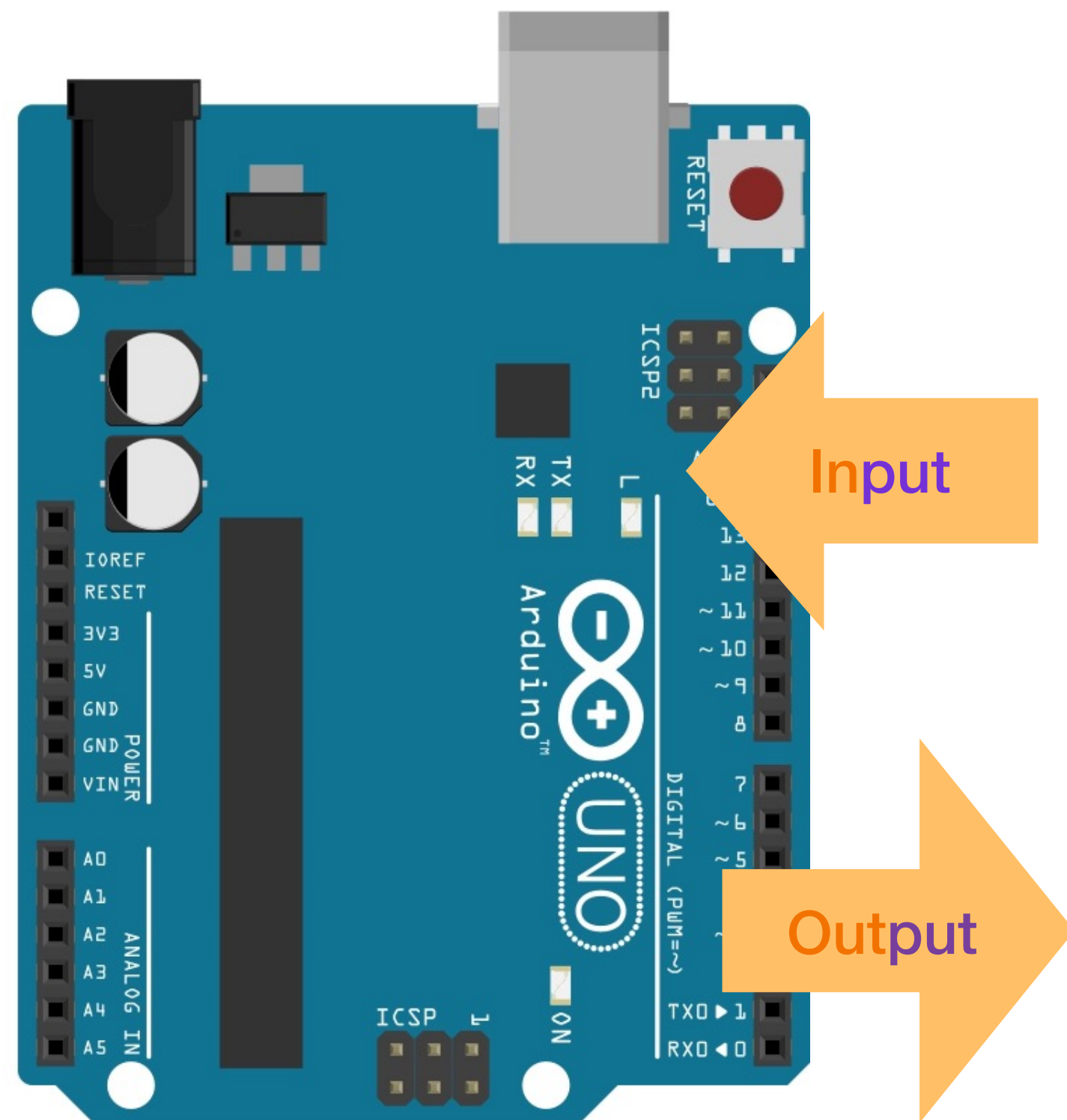When we discuss **INPUT** and **OUTPUT** we mean relative to our **ARDUINO**.



INPUT

Electric **SIGNAL** that moves **IN** to the **Arduino**

OUTPUT


Electric **SIGNAL** that moves **OUT** of the **Arduino**

DIGITAL


Refers to **SIGNALS**, **CIRCUITS** or **LOGICAL** systems that
have

ONLY TWO STATES
(0,1)

An **ON/OFF** SIGNAL.

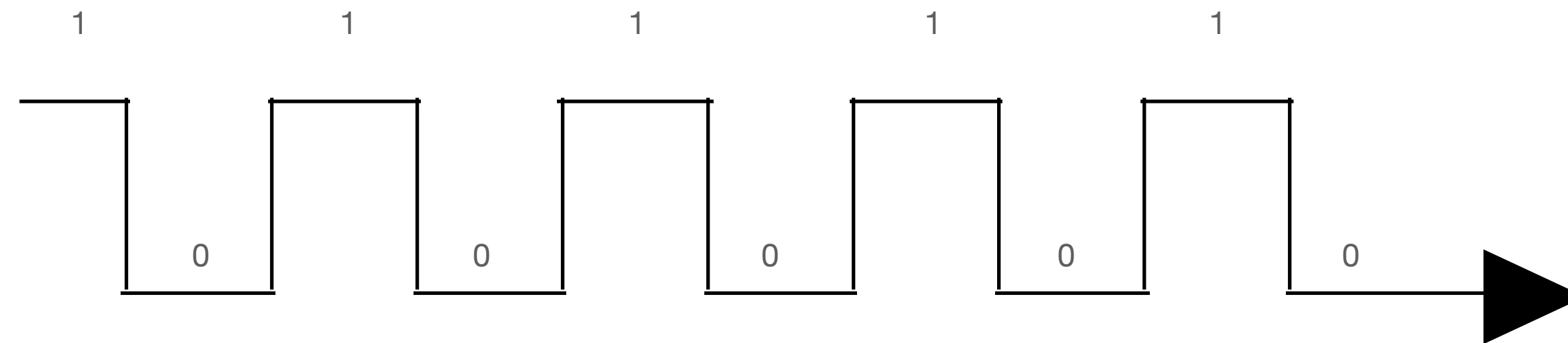


DIGITAL OUTPUT

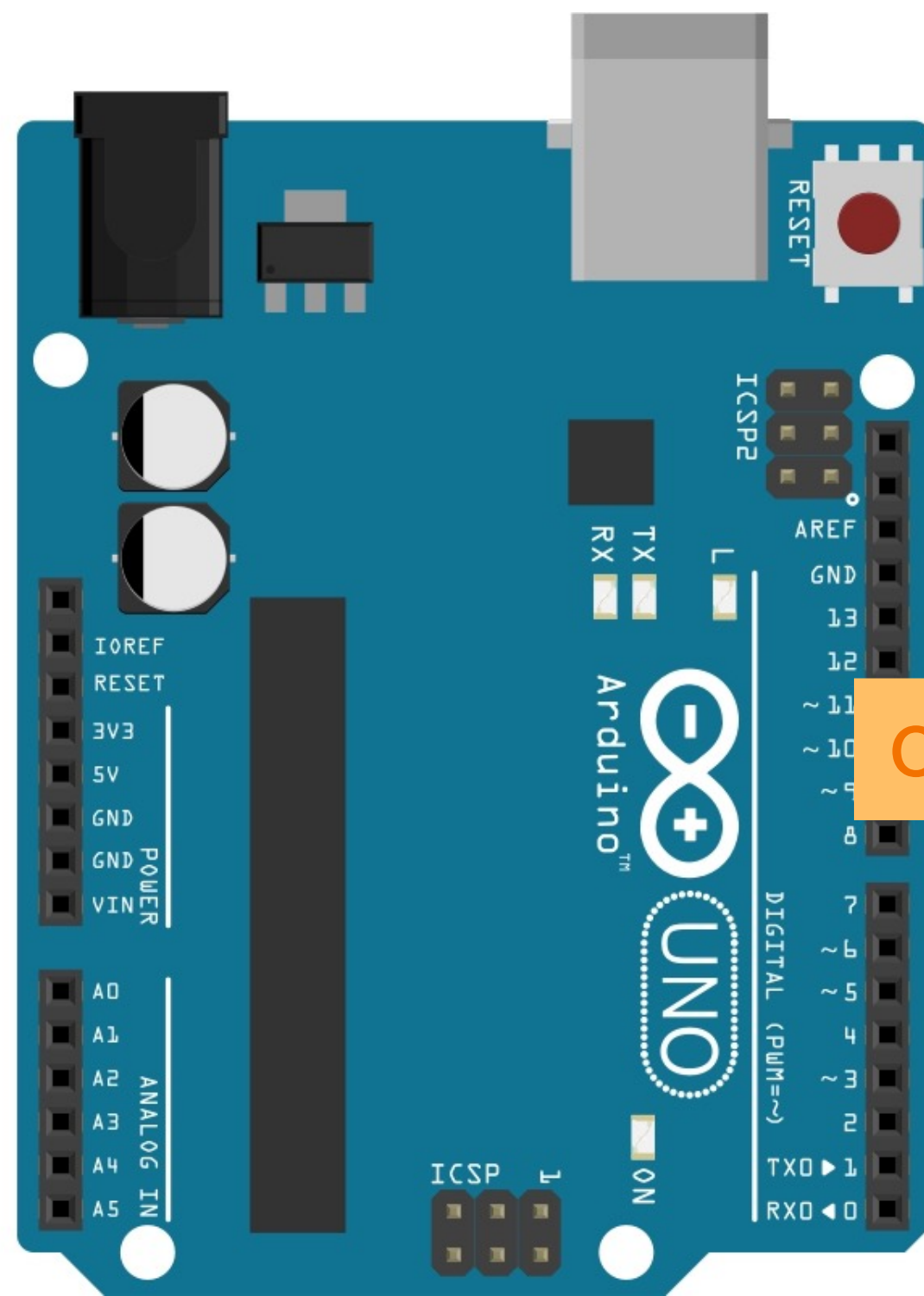

An **ON/OFF** SIGNAL that moves **OUT** of the Arduino

Output

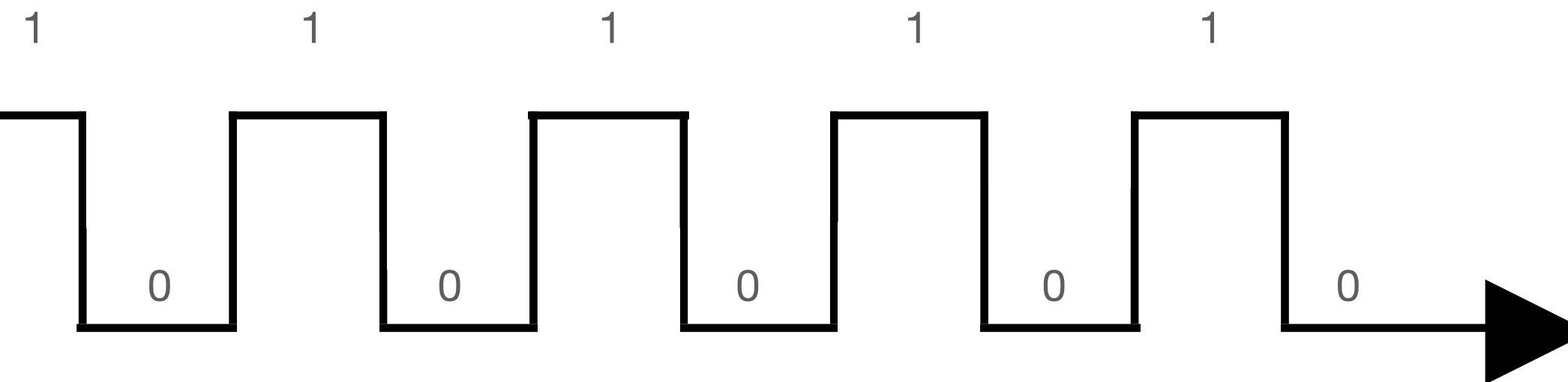

The CODE


Digital **Output** (**Blink** an LED)

```
digitalWrite( pin, state );
```


state = 0, 1 (LOW, HIGH)

The CIRCUIT

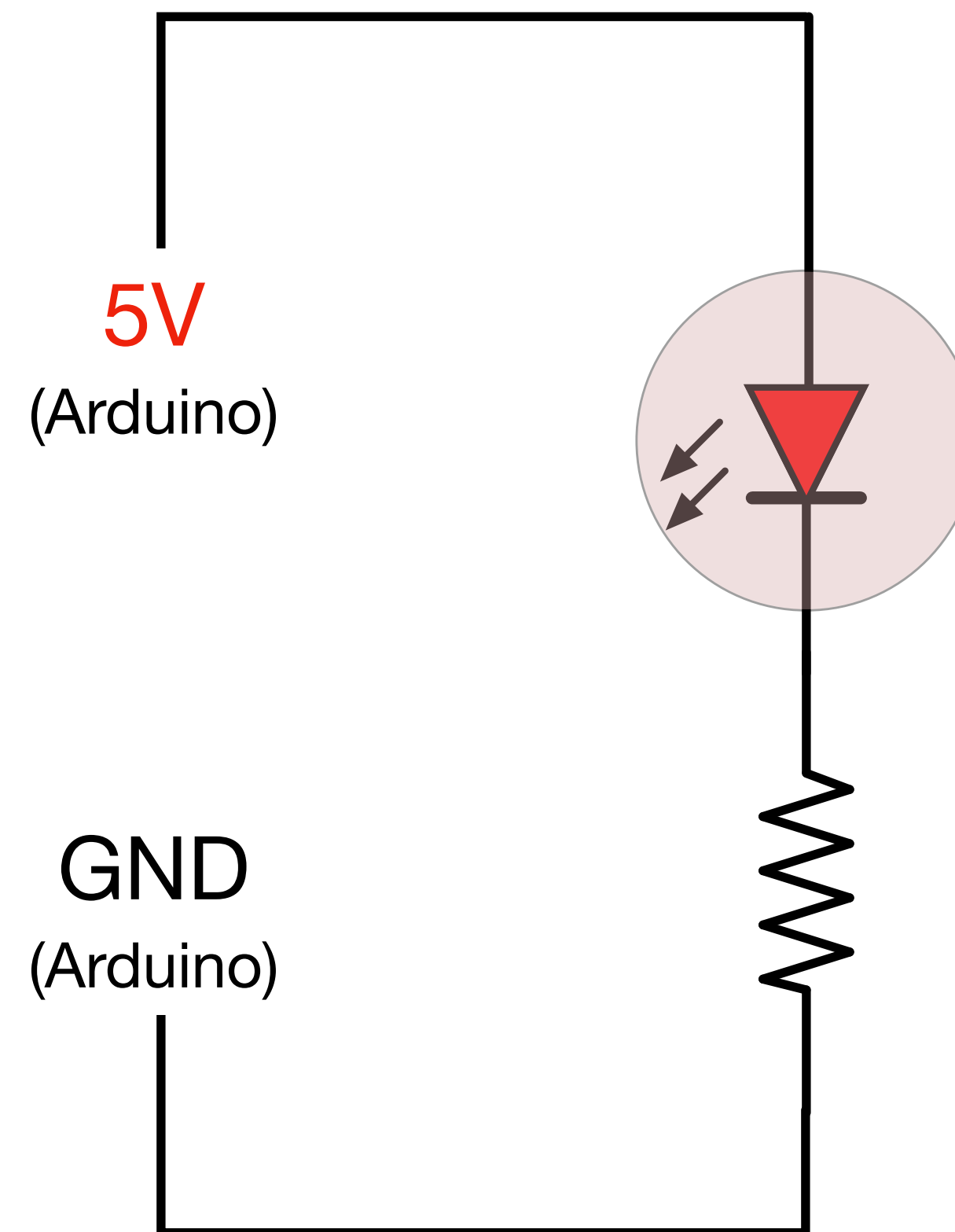
Here is the first circuit we built on a breadboard.




Let's rotate it on its side.

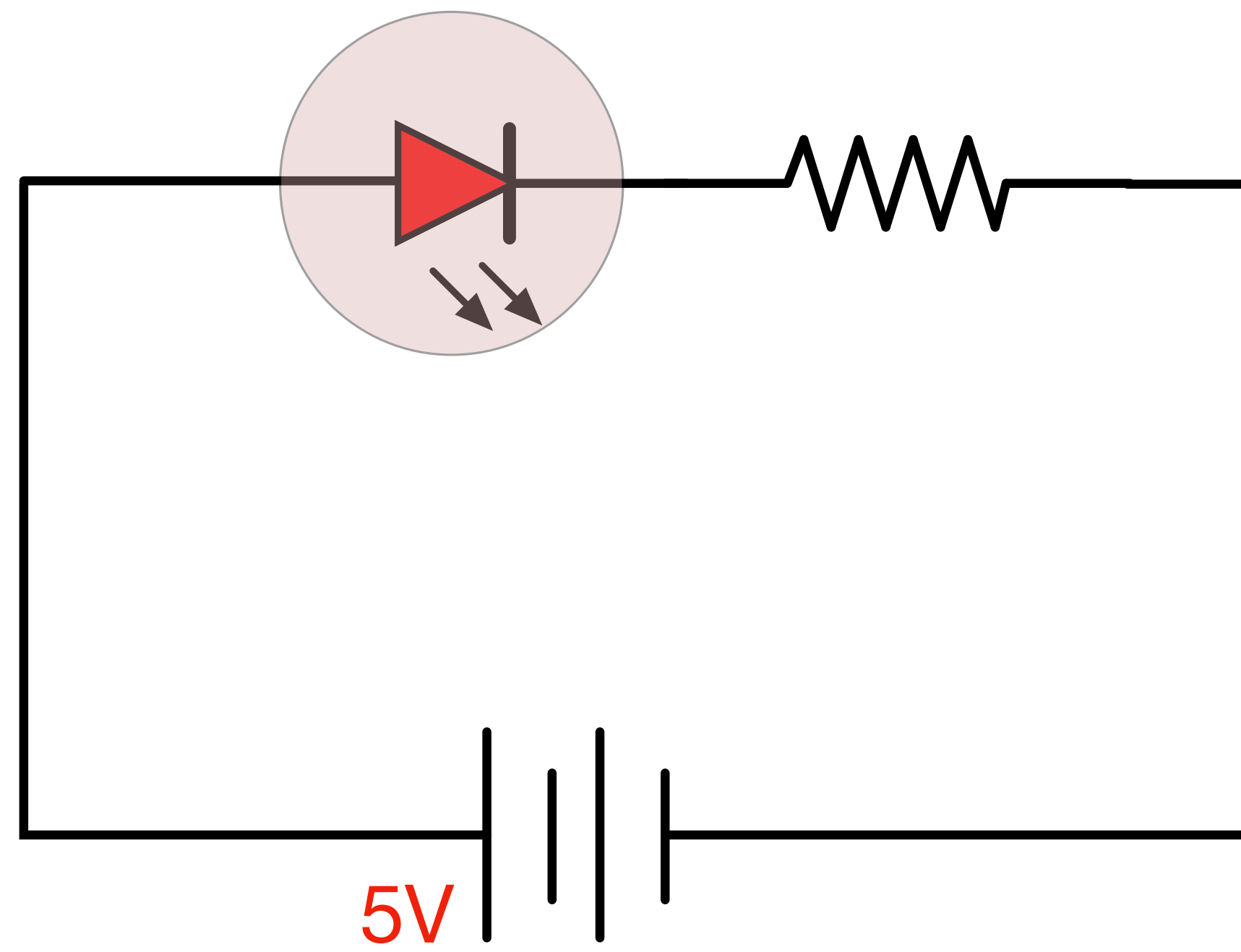

Let's rotate it on its side.

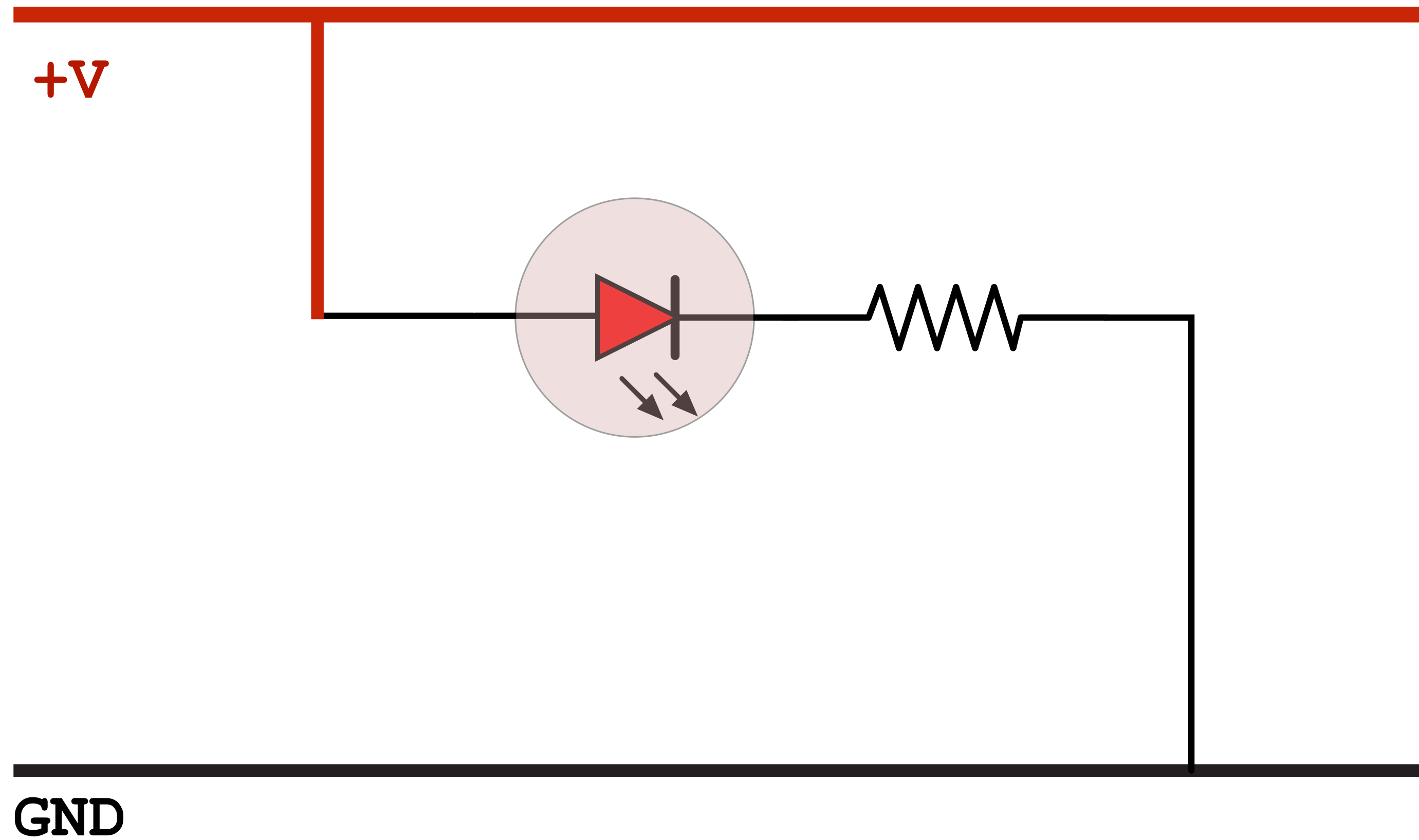


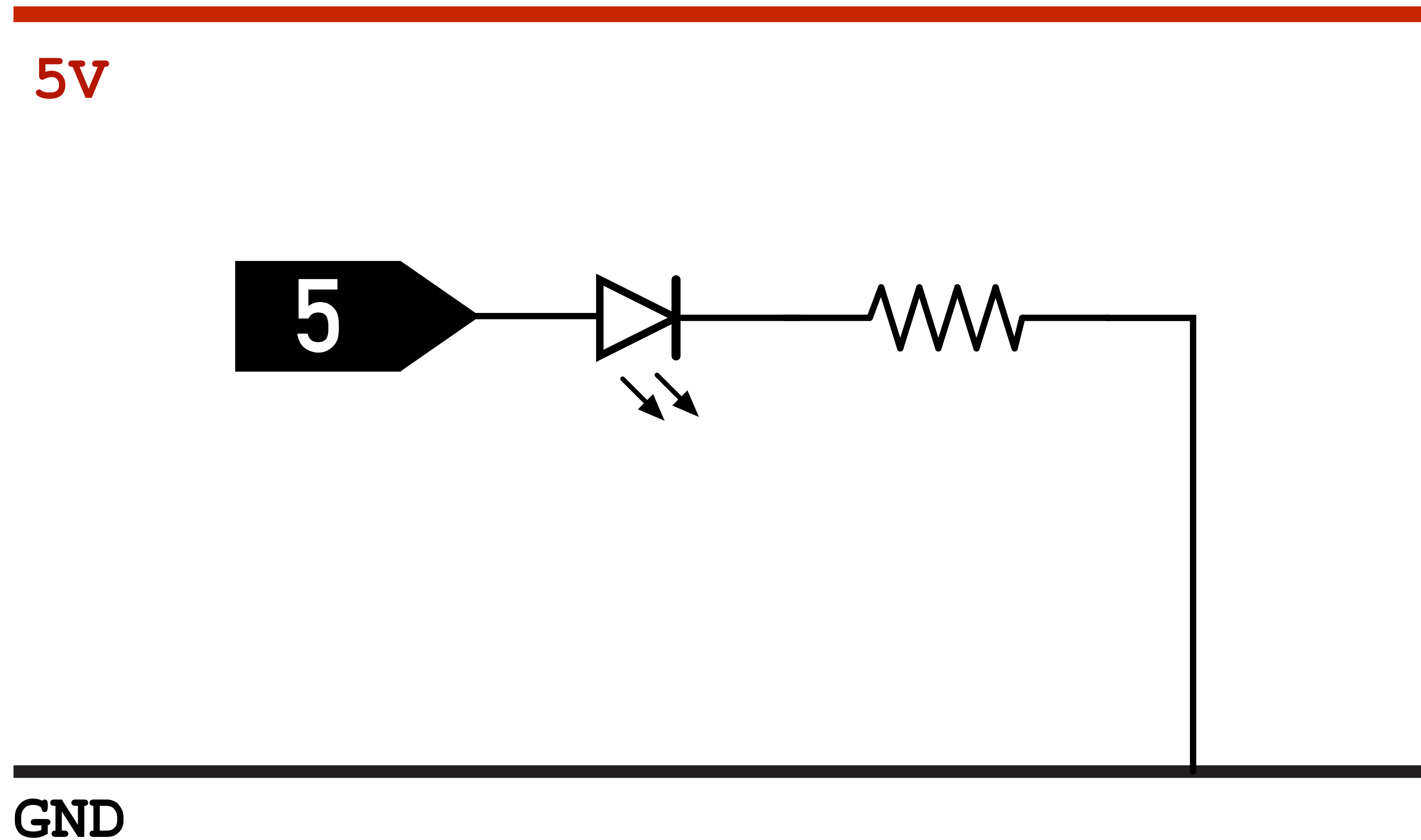**Then, remove the battery and connect
to Pin 5 on your Arduino.**




Let's compare ...

Goal Circuit

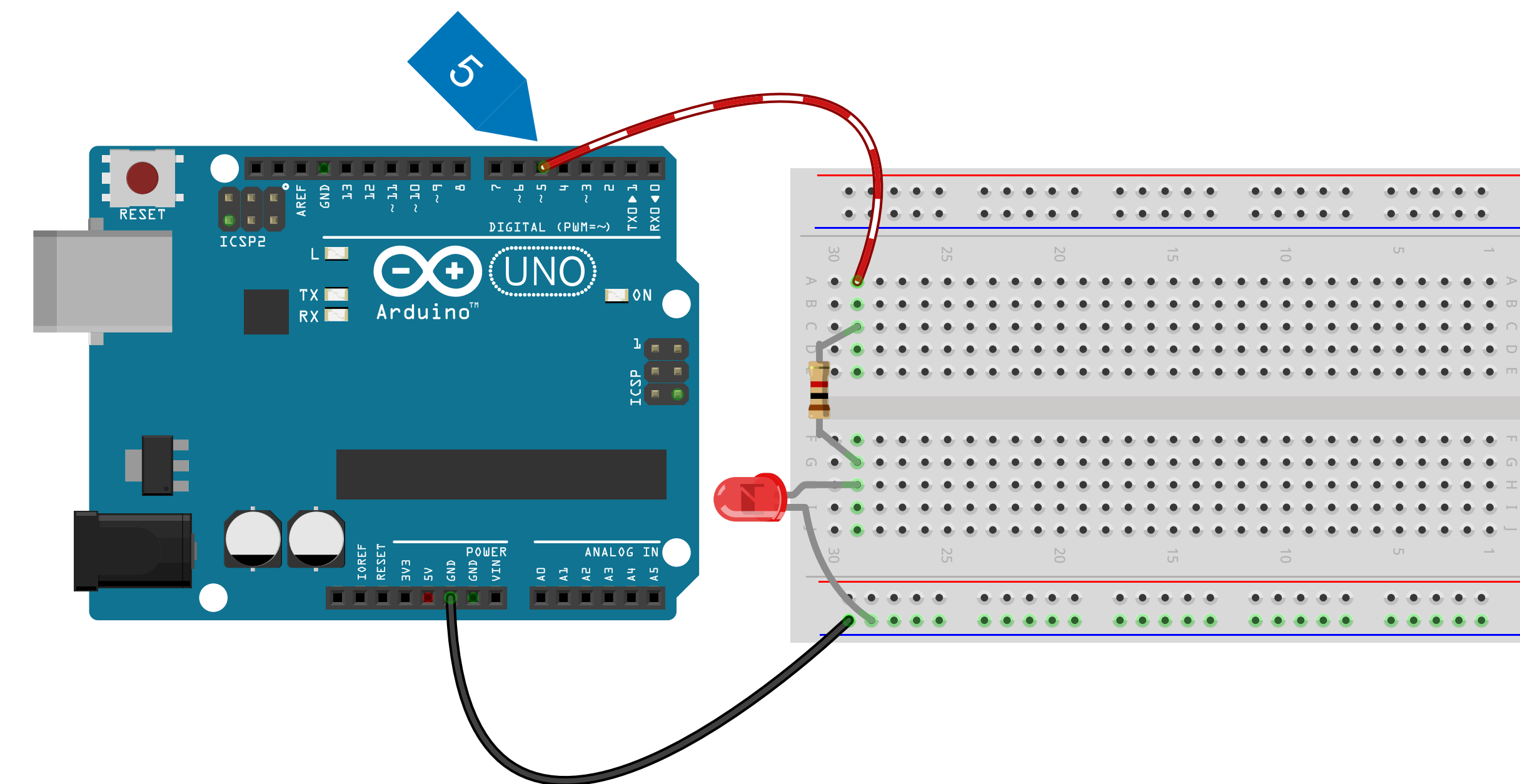


First Circuit:

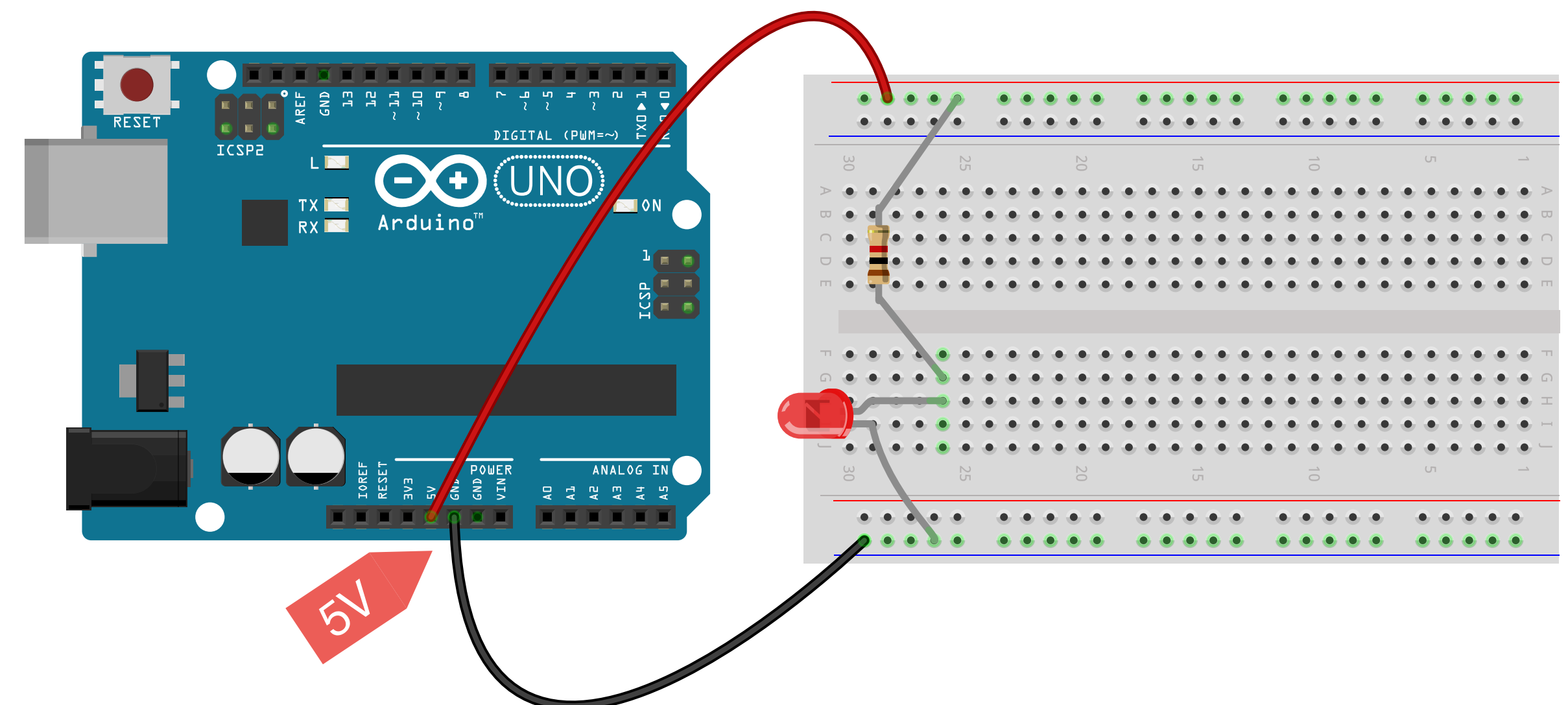


Arduino Digital Pins


BLINK circuit - **POWER** from a PIN!

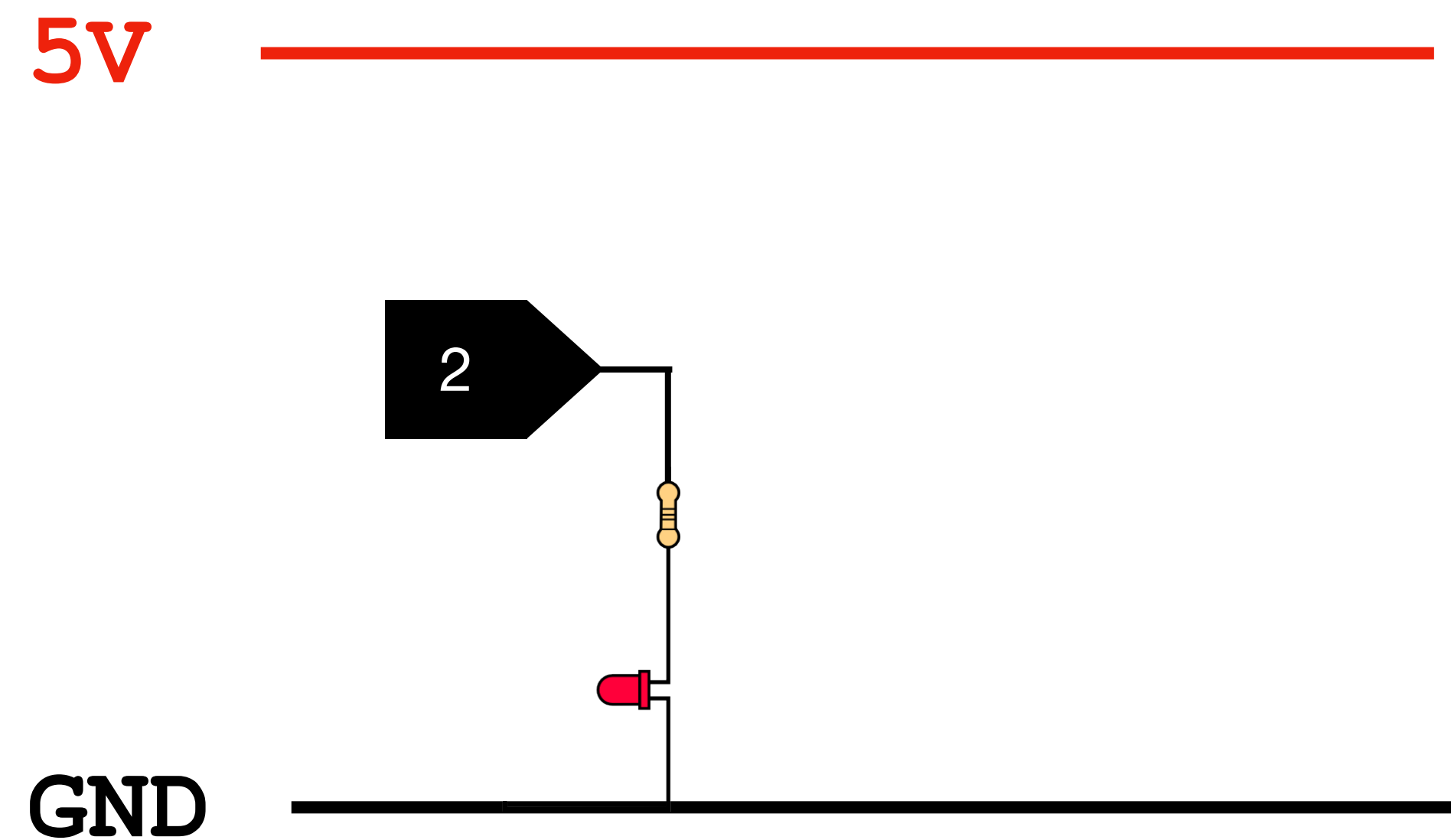

Intro circuit - continuous **POWER**

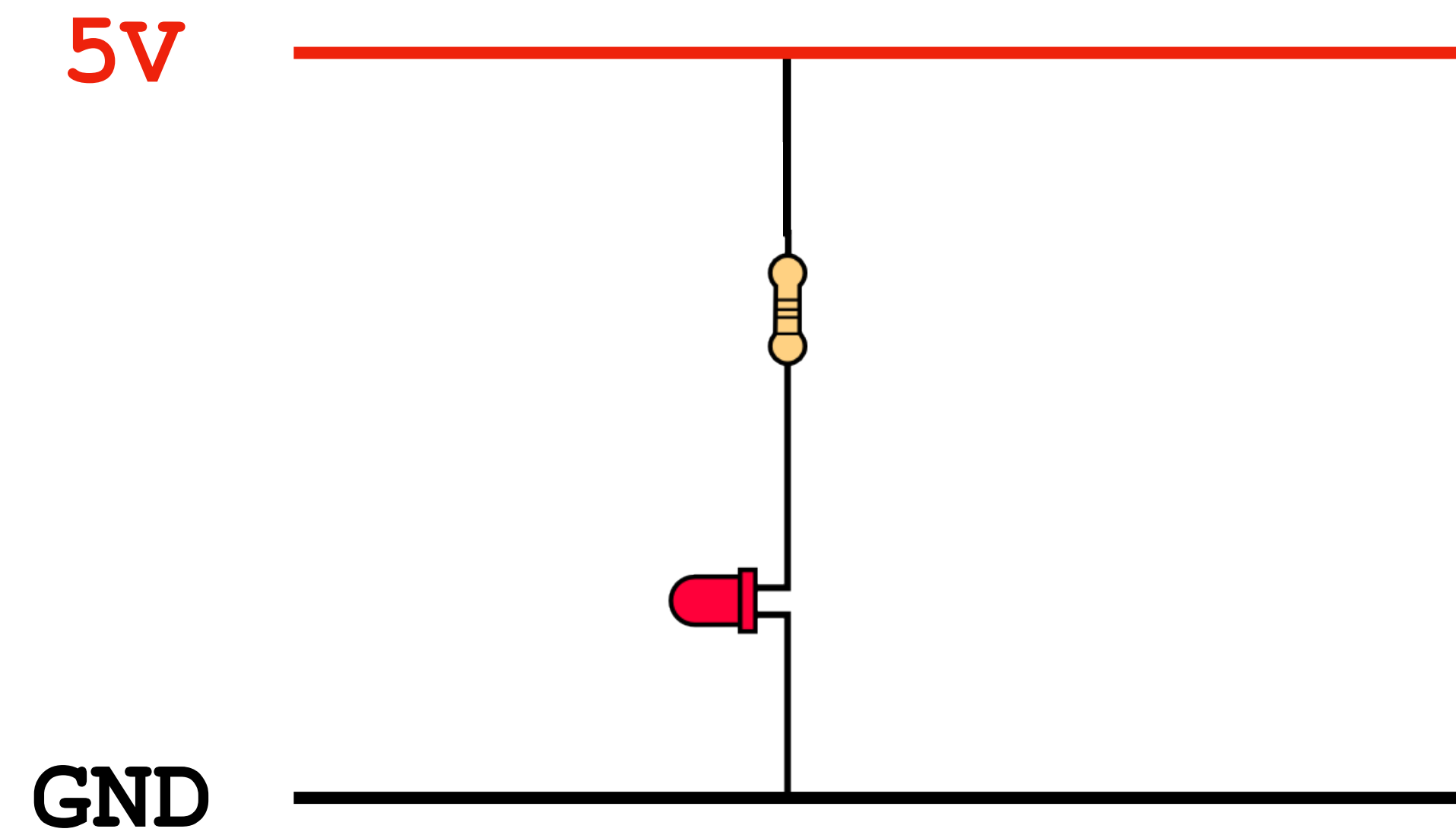

Its a simple mod

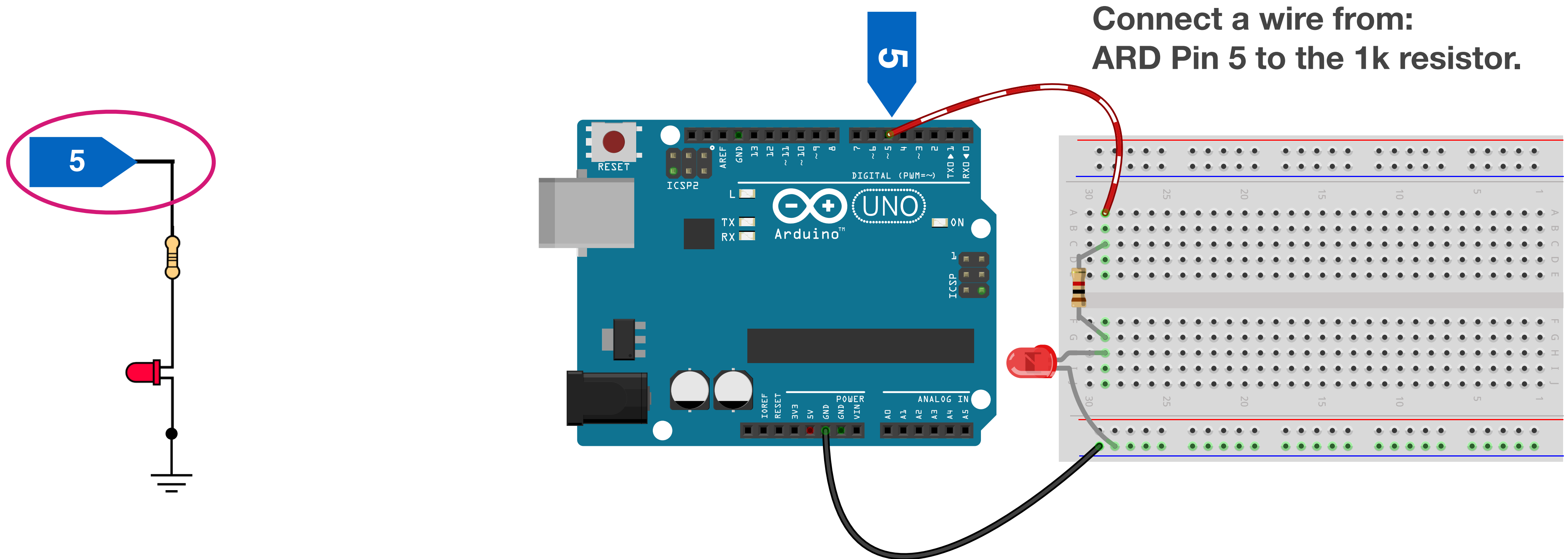

fritzing


Let's Add Code

(Making things BLINK)

Let's Upload Code


01-simpleBlink.ino

What's Going ON ?

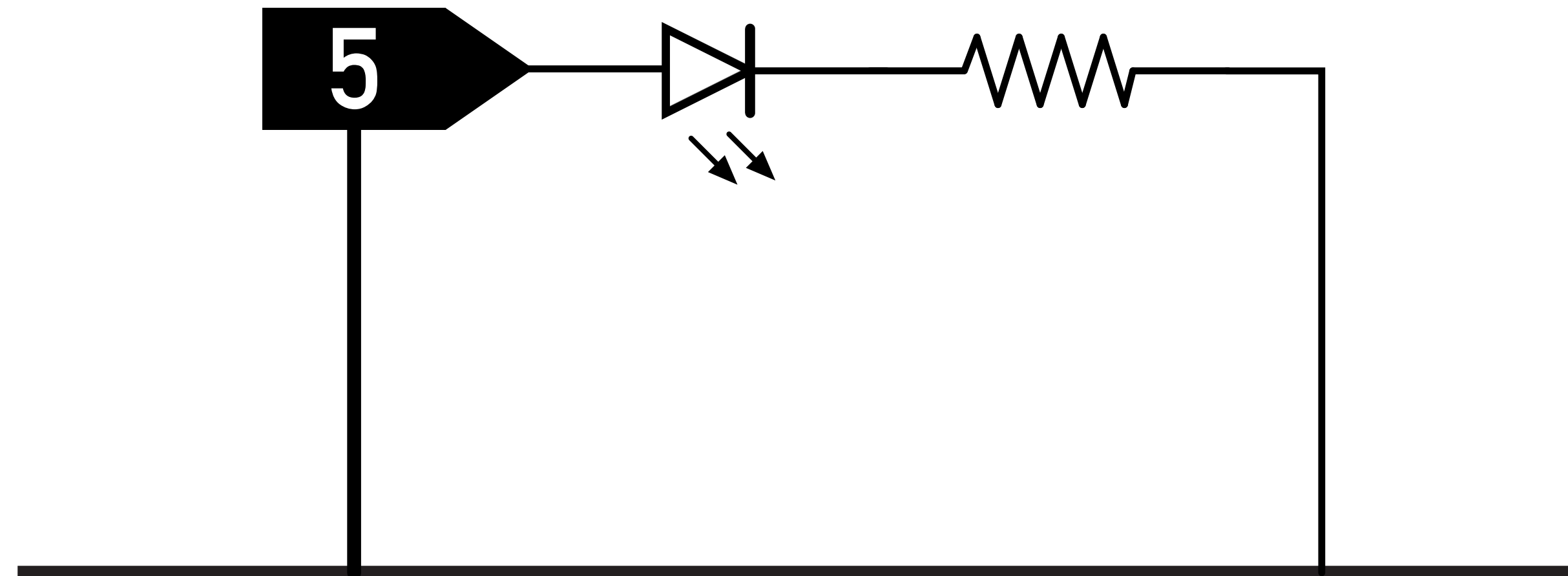

```
digitalWrite(5, LOW);
```


What's Going ON ?

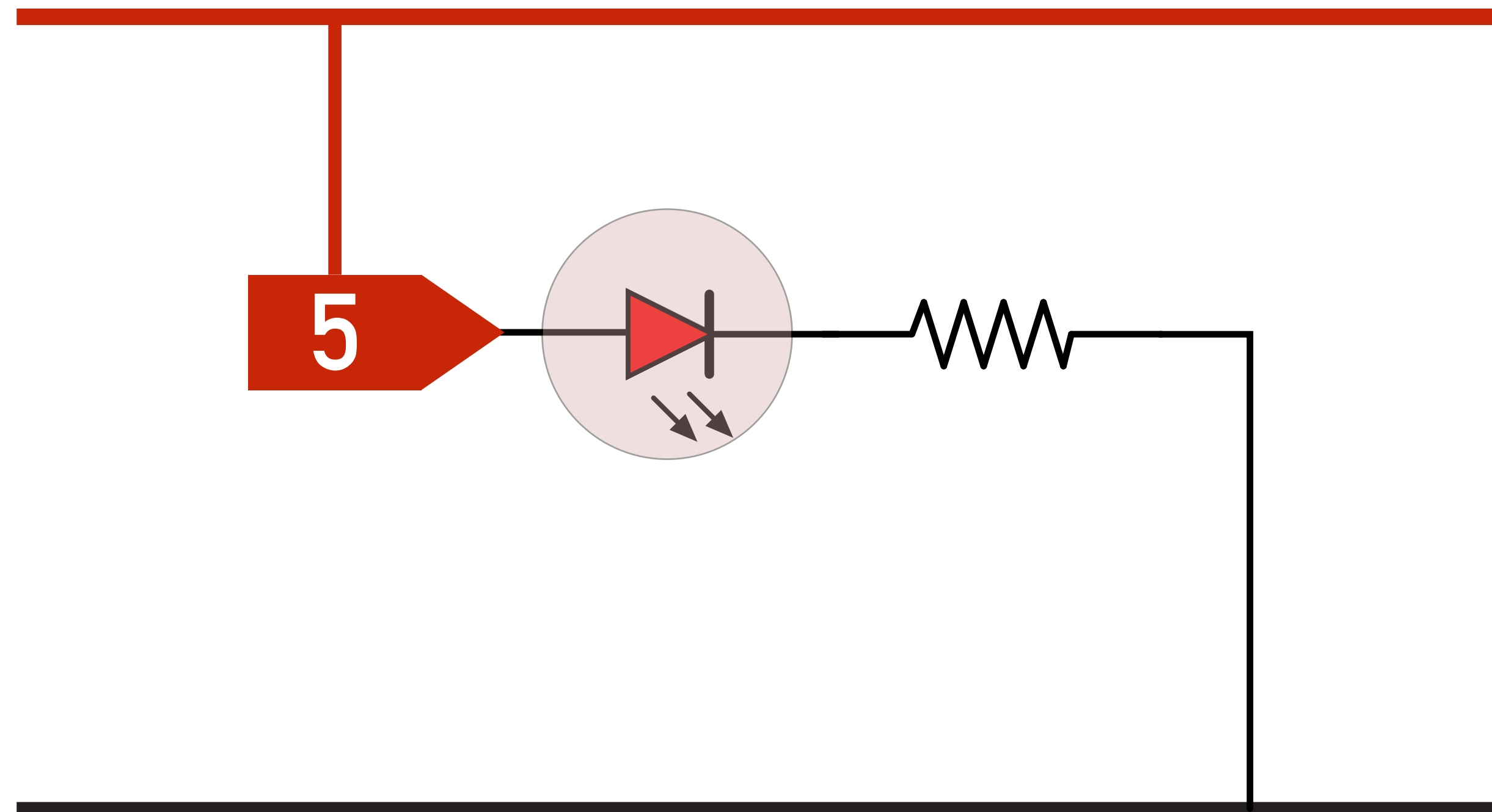

```
digitalWrite(5, HIGH);
```


One more time ...

Digital pins are independent waterfalls.

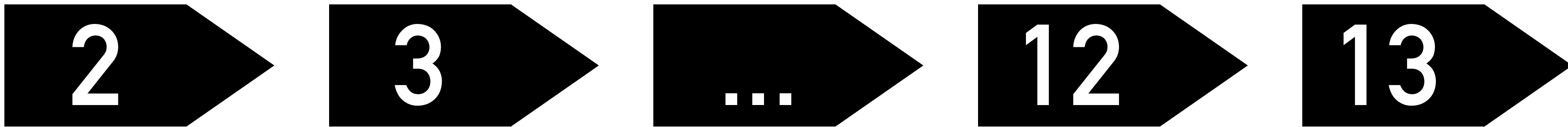

One more time ...

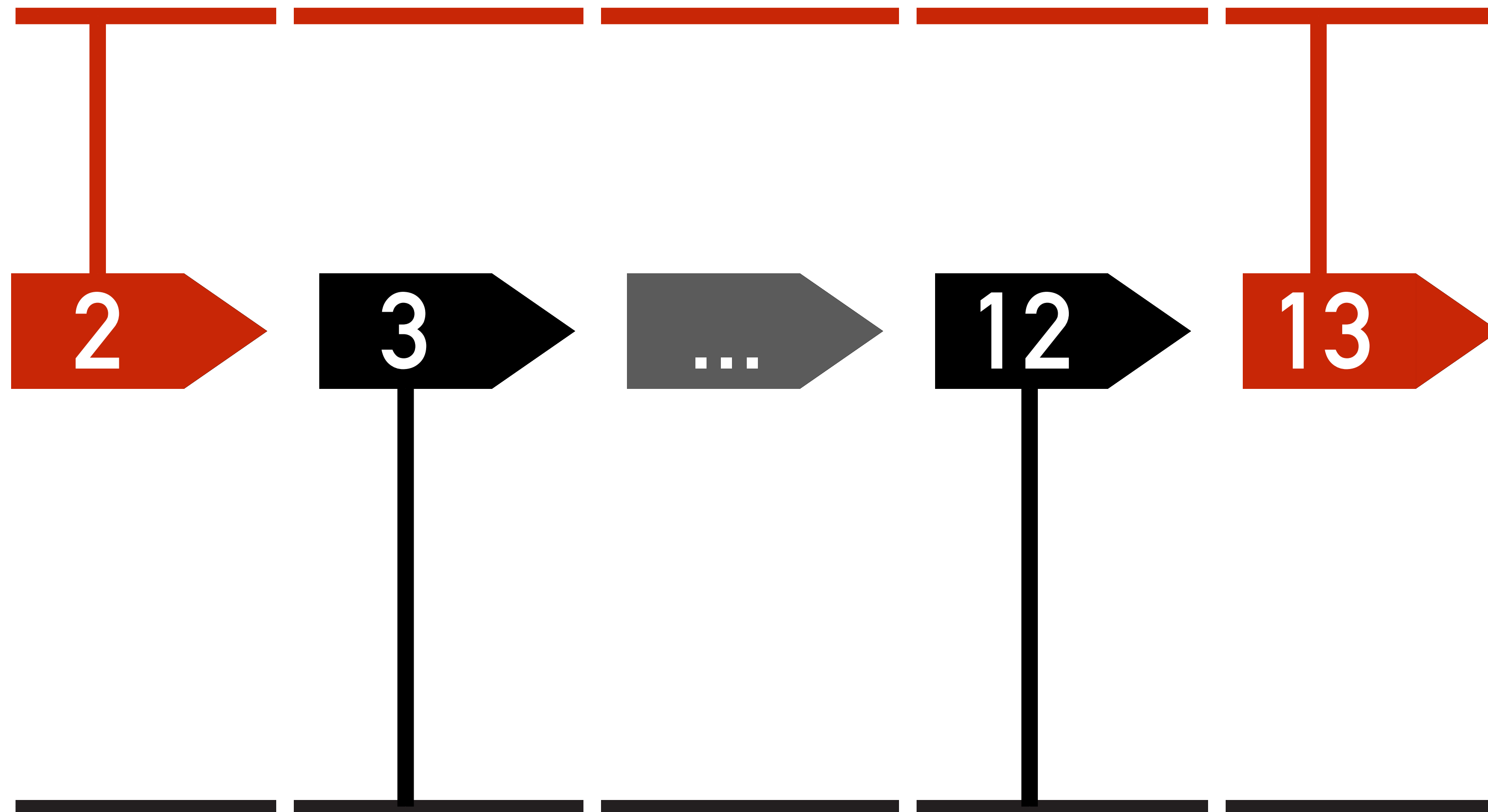
Pin VOLTAGE can be set with words <CODE>.




Going beyond

(multiple LEDs)


Let's Blink two LEDs

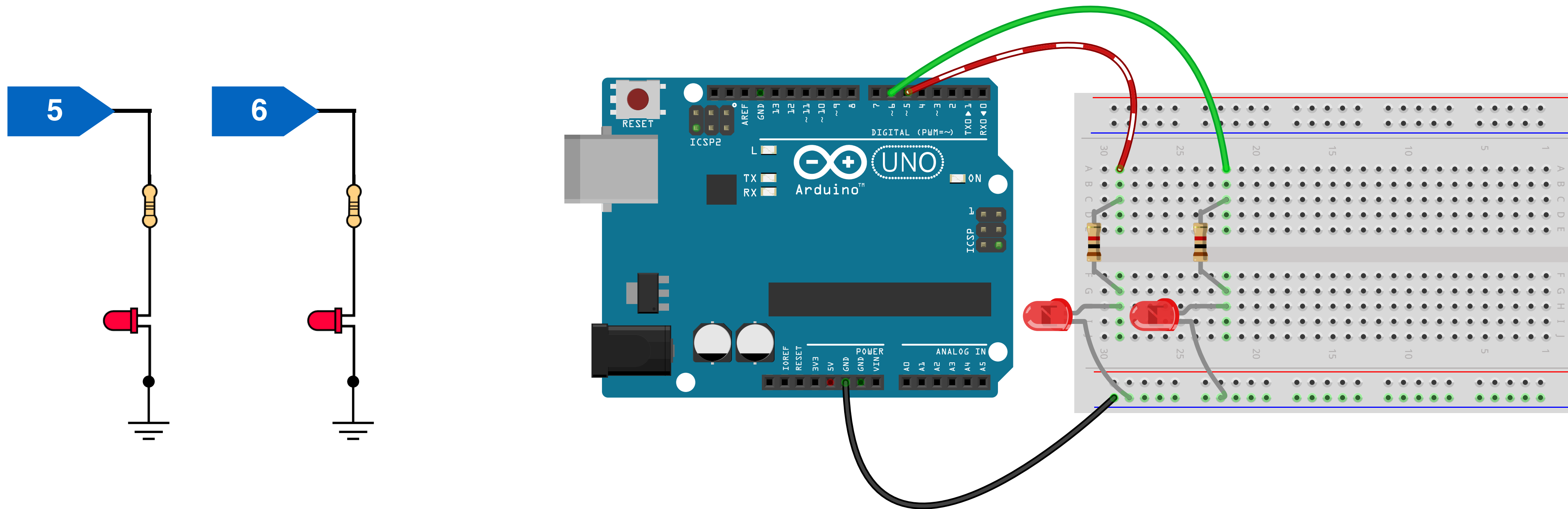

Let's break this build down:

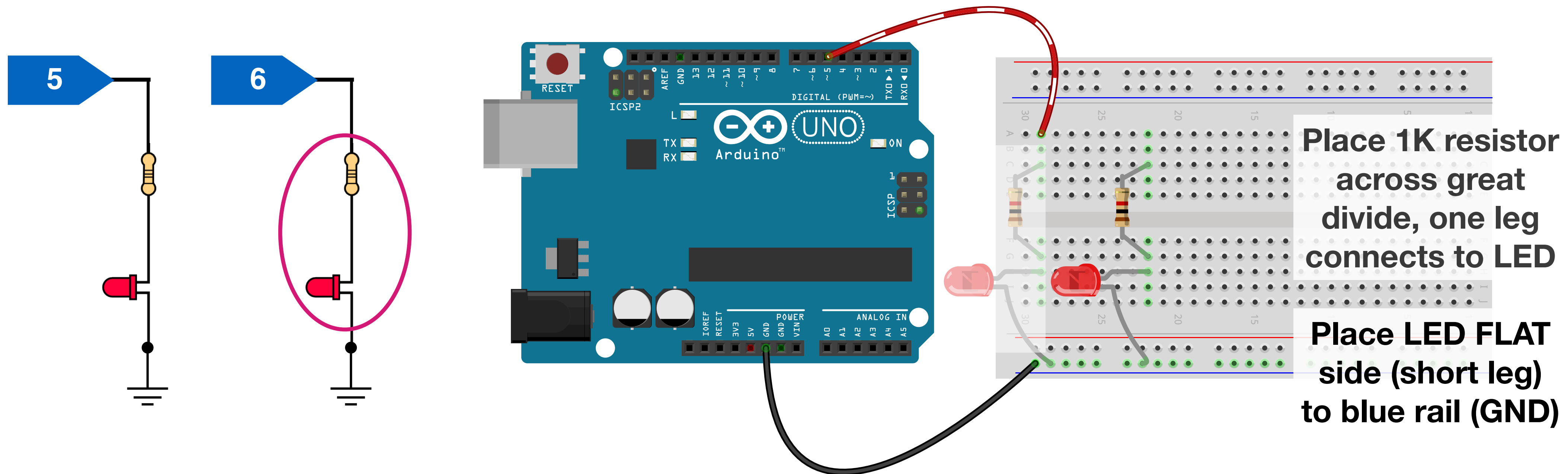



Let's Blink two LEDs

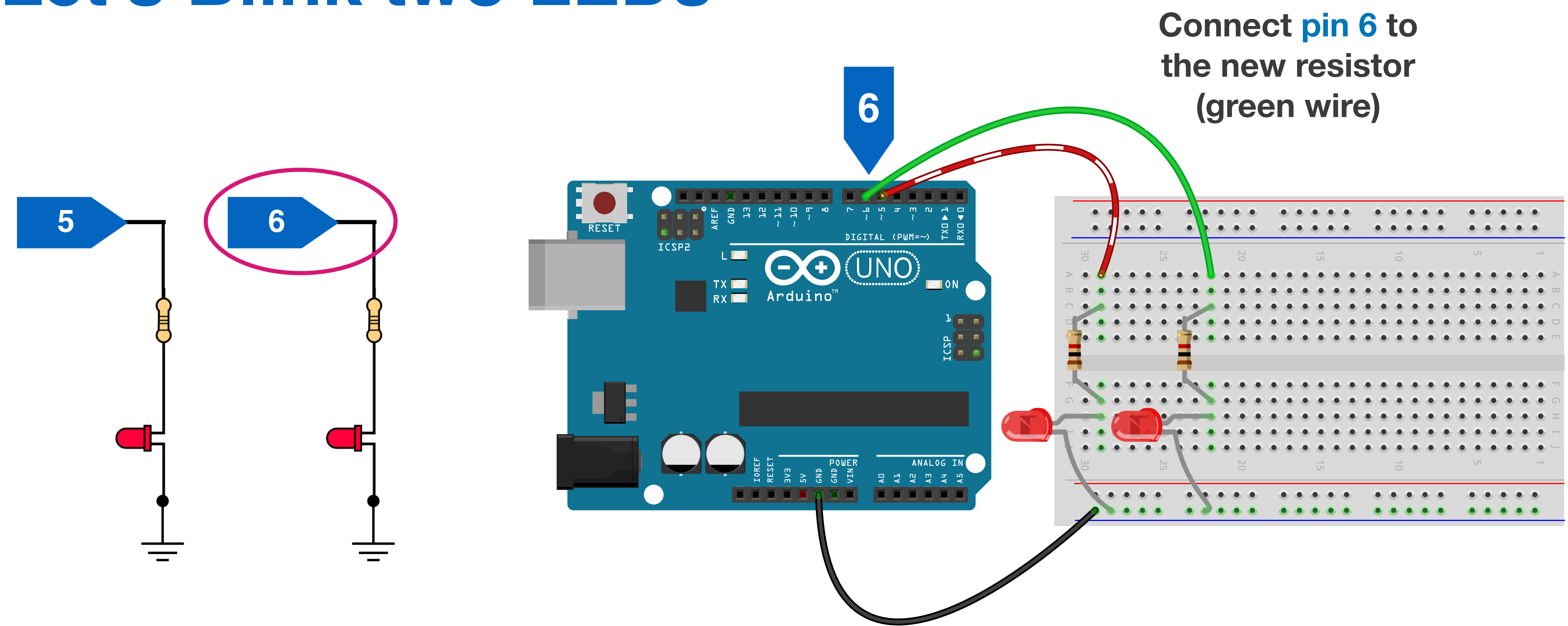

Can we extend our code to talk to **TWO LEDs?**

If it goes sideways
`02-blinkTwo.ino`

Three?

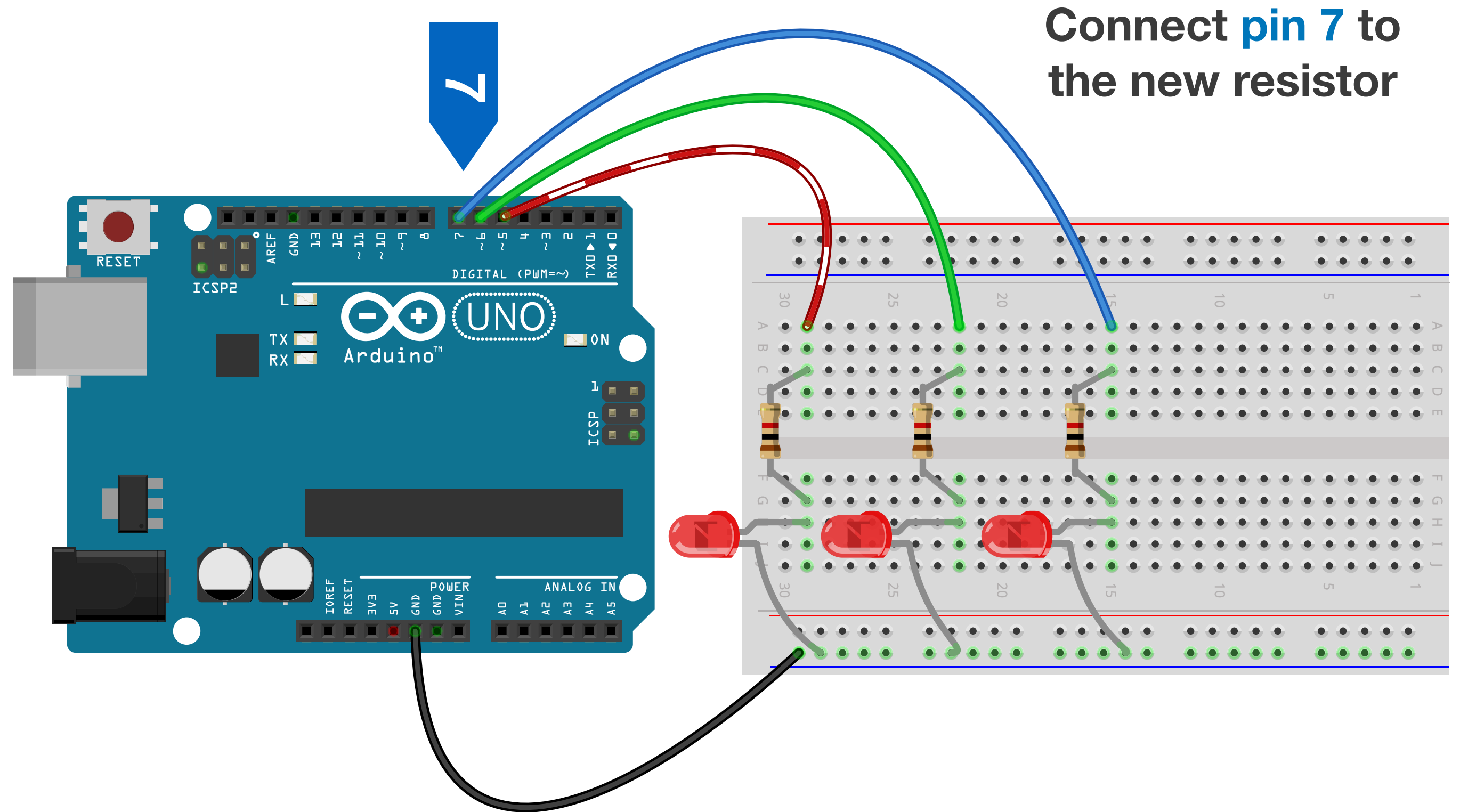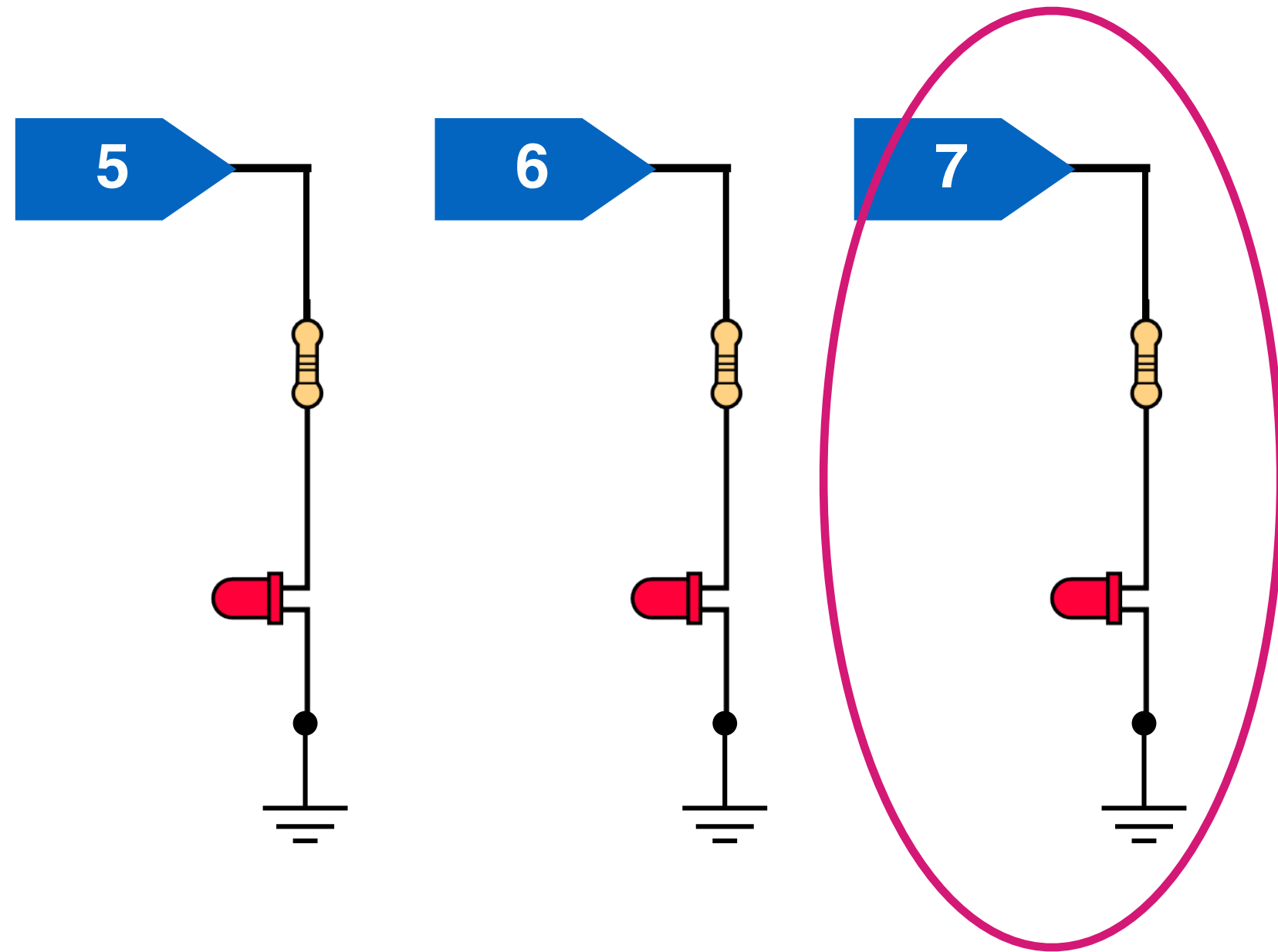


**Let's upload
3-led code**

03-blinkThree.ino

CIRCUIT **variations** **R****G****B**

GOAL — Let's ADD an RGB circuit


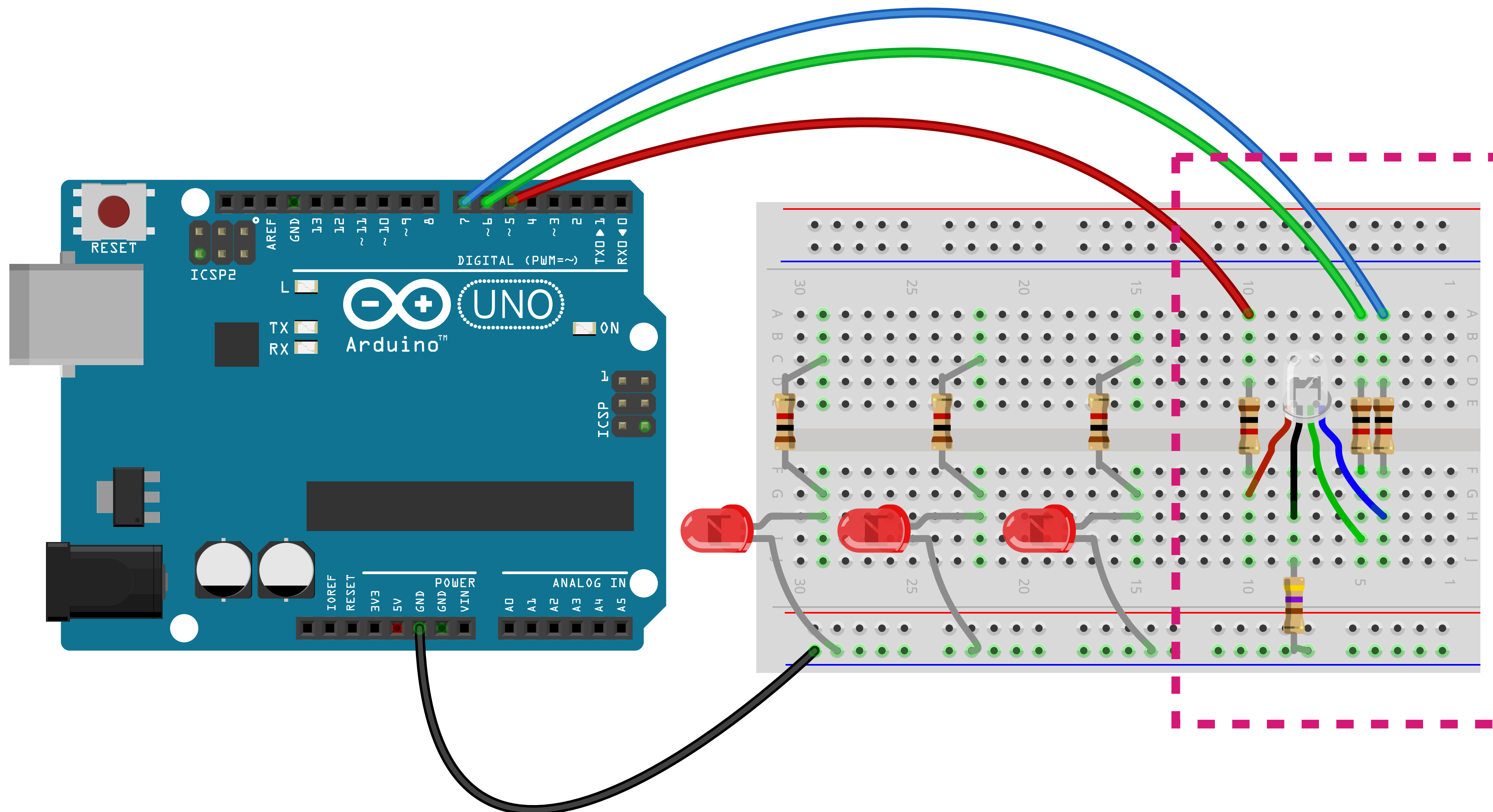
For location only — Keep RGB to the right!



RGB led



RGB led

New part — RGB LED

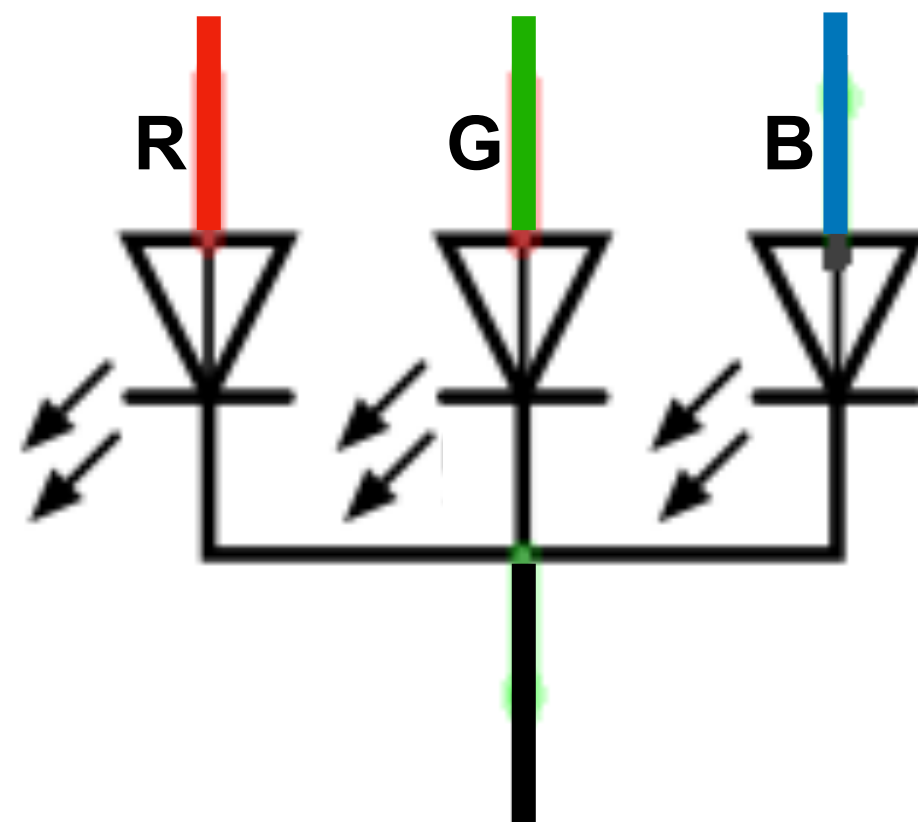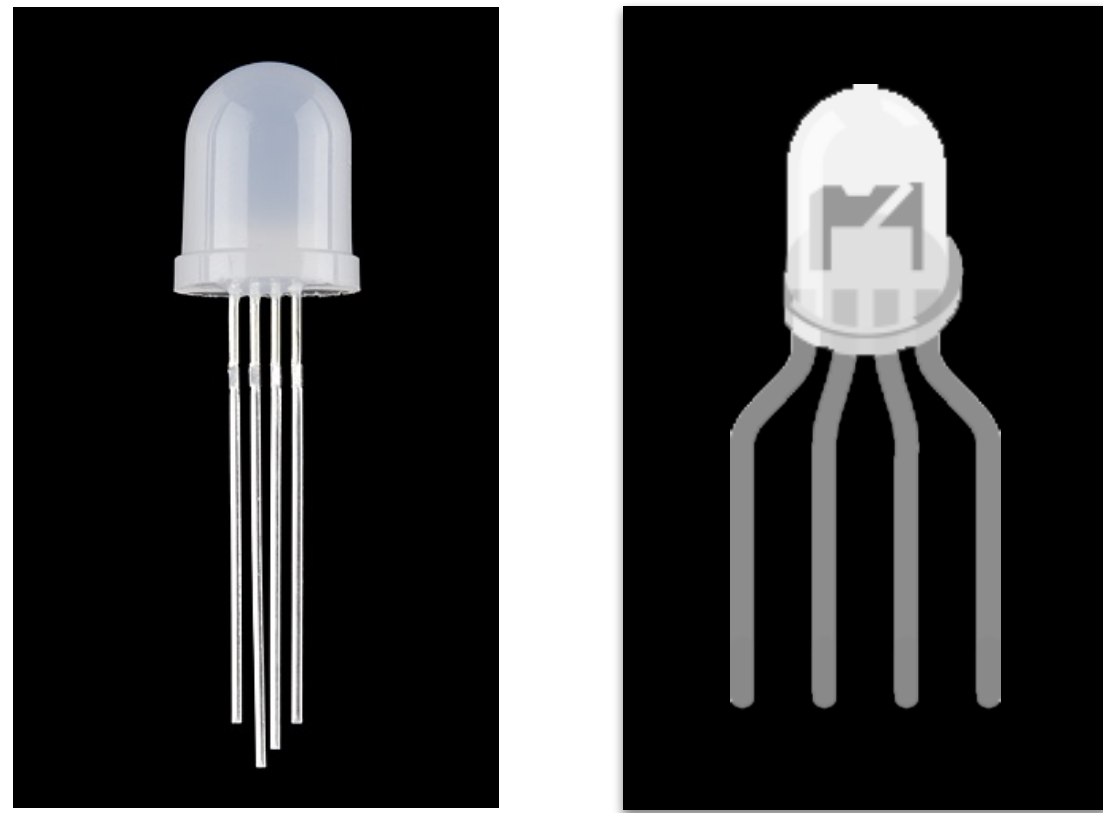

- **RGB LEDs want to GLOW (eventually — millions of colours)**
- like single LED cousins — they want a small amount of power — and they want it going in the right direction
- they want protection — from current limiting resistors

RGB led

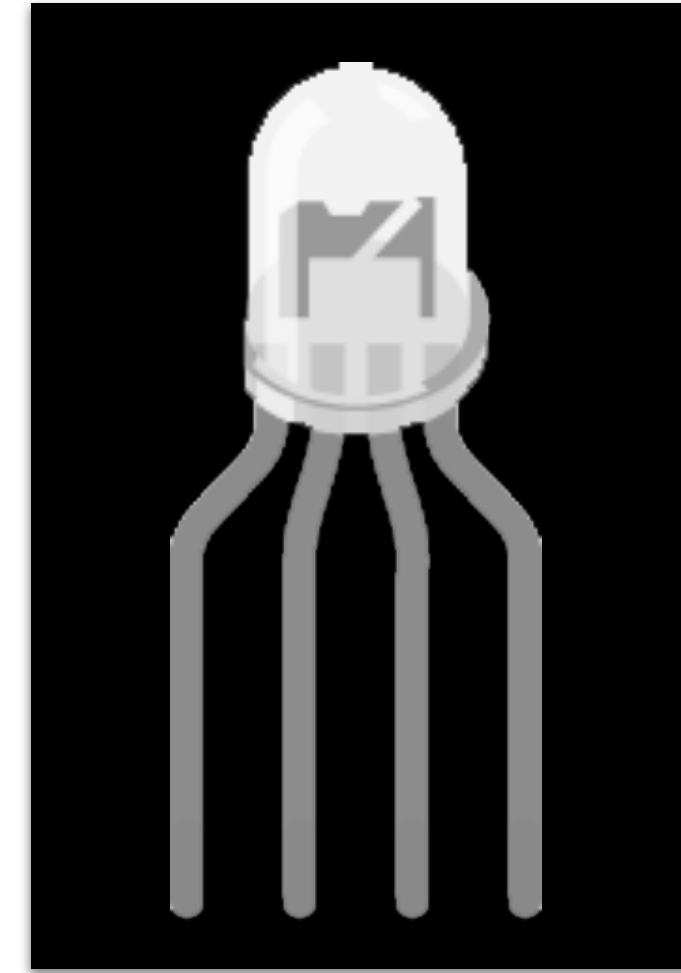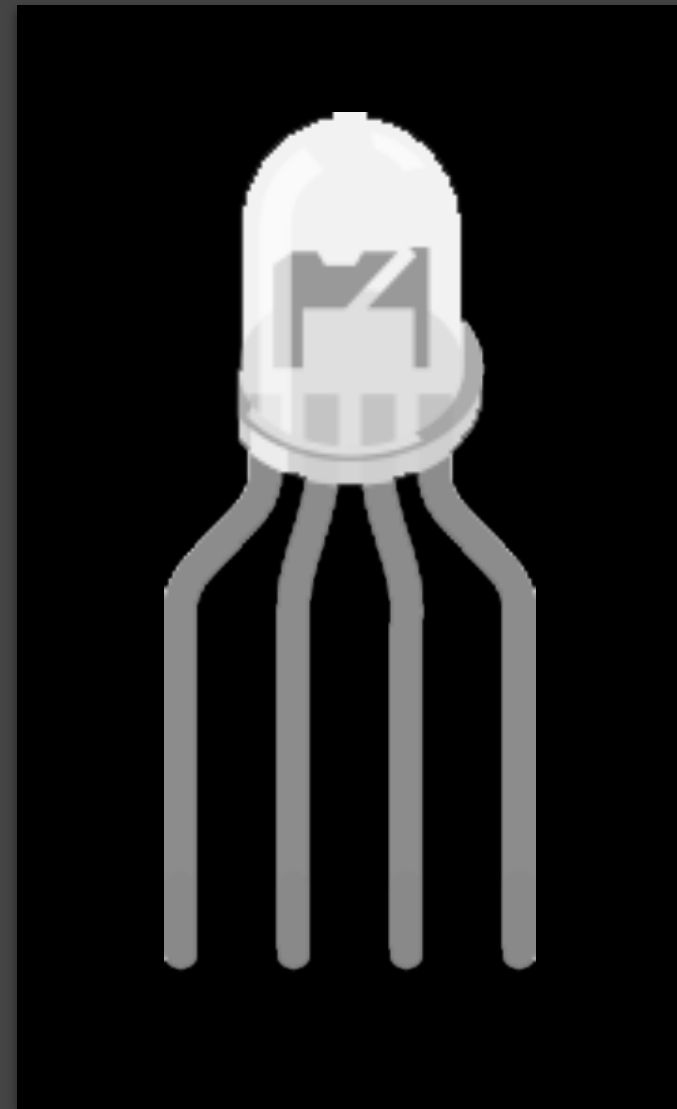


RED
GND
GREEN
BLUE

**GROUND (GND)
is longest!**

Let's **ADD** an **RGB** circuit.

- Place a **470 ohm** resistor from GND leg to blue rail (GND).
- Put a **1K** on each **RGB leg, across great divide.**
- Connect 1k resistors to a strip of tie points (**not to power rail**).

NOTE - single color LEDs not shown

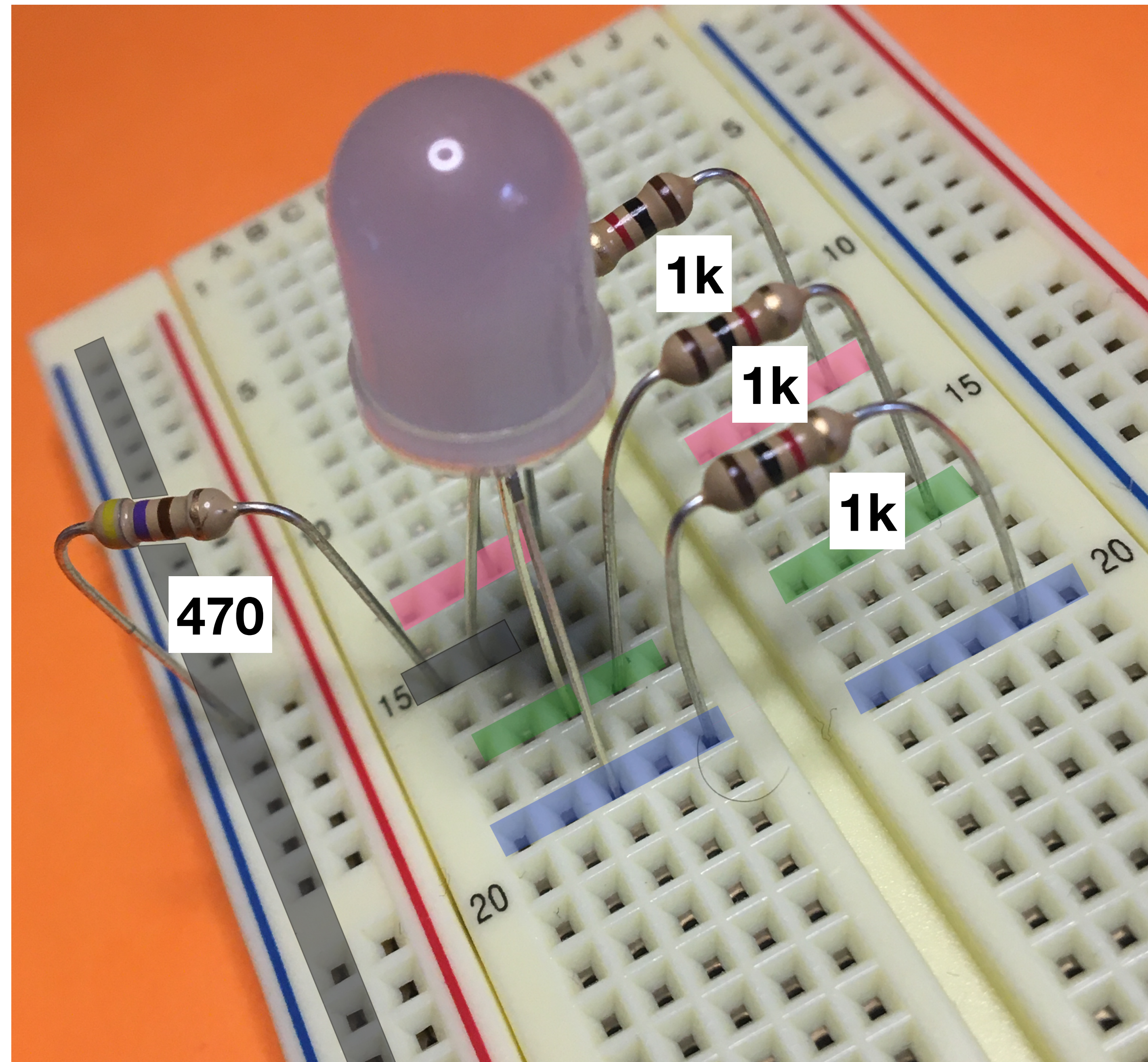

Place this on
right side
of your board

Explore :


Power up your
Arduino.

Upload first code
from today.

`01-simpleBlink.ino`

Connect **pin5** to the
RED (left) leg of
your **RGB** led.

(then move wire to **G** and **B** too)

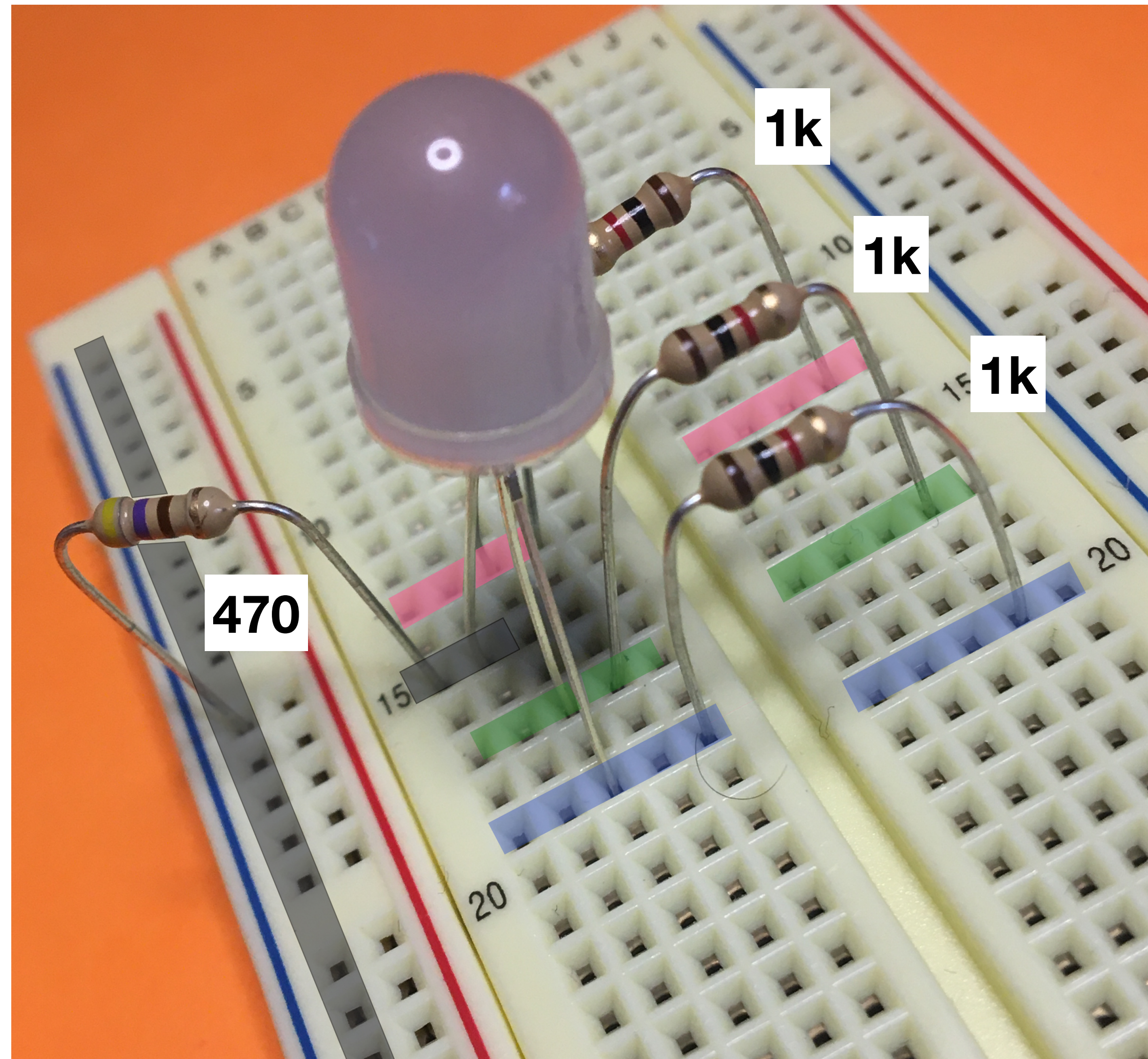


R**G****B** **C****O****D****E**

variations

5

6

7

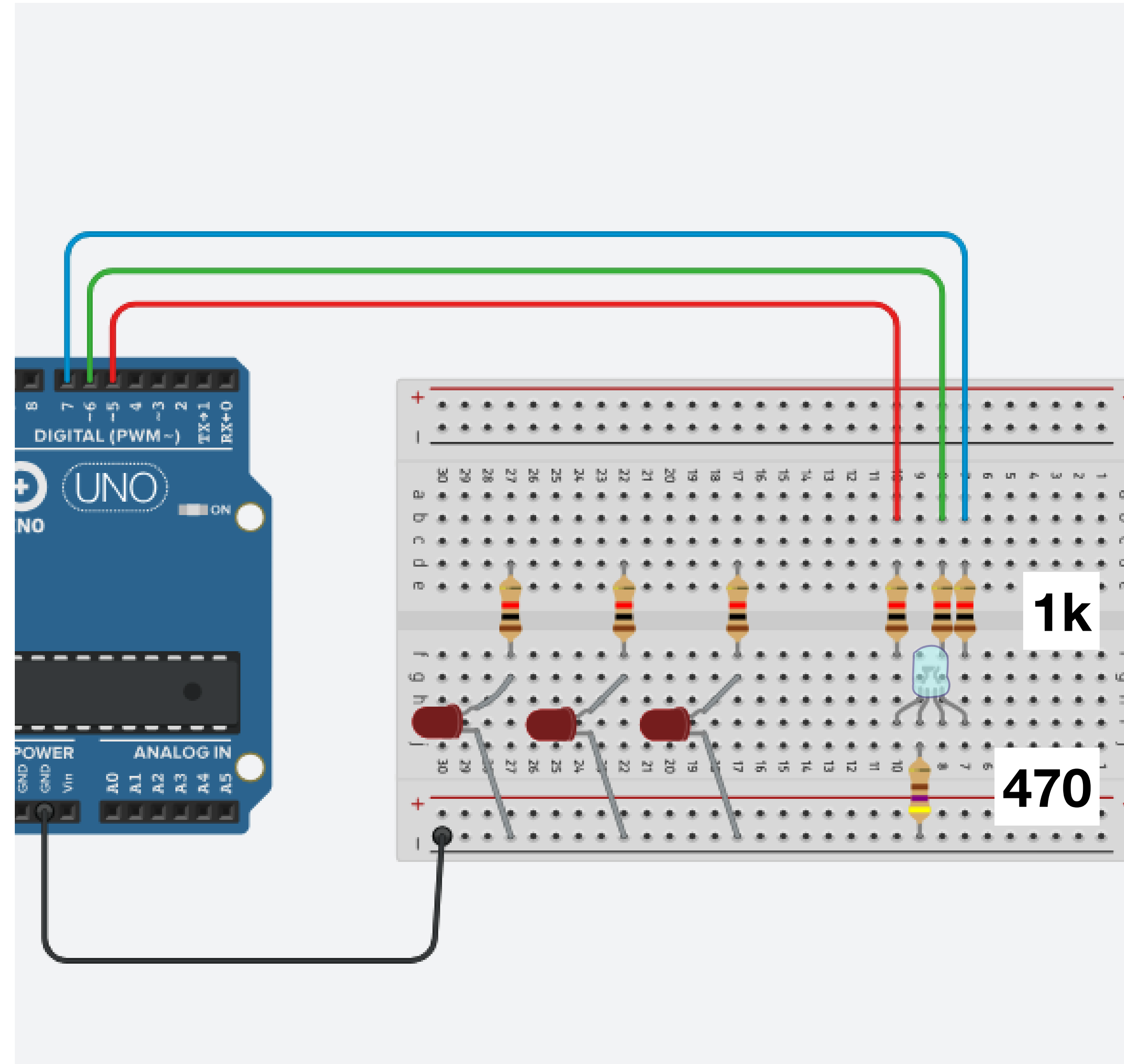

**Let's re-upload
3-led code**

`03-blinkThree.ino`

03-blinkThree.ino

**Can you change this code
to blink two (2) colours
at a time?**