

tangible

Digital OUTPUT

Tangible Matrix

Context	DIGITAL	ANALOG
INPUTS	BUTTON	POTENTIOMETER photoCell
OUTPUTS	LED BLINK	LED FADE

Digital OUTPUT

Context	DIGITAL	ANALOG
INPUTS	BUTTON	POTENTIOMETER photoCell
OUTPUTS	LED BLINK	LED FADE

INPUT / OUTPUT

When we discuss **INPUT** and **OUTPUT** we mean relative to **ARDUINO**.

INPUT

Electric **SIGNAL** that moves **IN to** the **Arduino**

OUTPUT

Electric **SIGNAL** that moves **OUT of** the **Arduino**

DIGITAL

Refers to **SIGNALS**, **CIRCUITS** or **LOGICAL** systems that

have

ONLY TWO STATES

DIGITAL OUTPUT

An **ON/OFF** SIGNAL that moves **OUT** of the Arduino

The CODE

Digital **Output** (**Blink** an LED)

```
digitalWrite( pin, state );
```

state = 0, 1 (LOW, HIGH)


REFERENCE - Card in your kit.

Digital Output

CONTEXT

	Digital	Analog
Input		
Output		

CIRCUIT

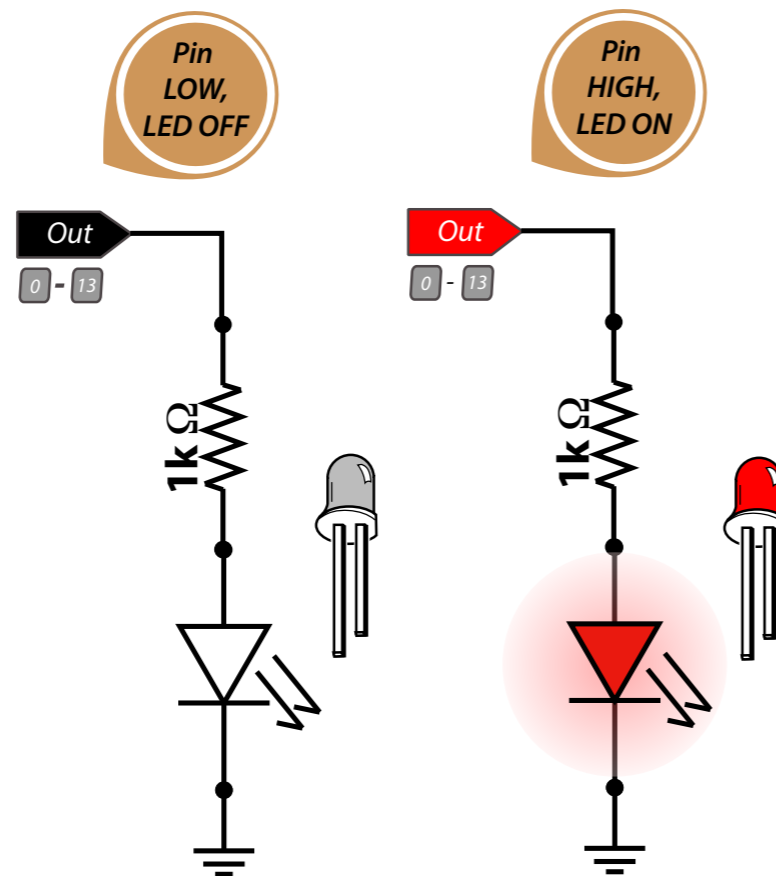

COMMAND

```
digitalWrite ( pin, state );
```

pin = 0-13

state = HIGH (1, 5V) , LOW (0, GND)

CODE

```
int ledPIN = 13;
```

```
void setup() {
```

```
    pinMode( ledPIN, OUTPUT );
```

```
}
```

```
void loop() {
```

```
    digitalWrite( ledPIN, 1 );
```

```
    delay(1000);
```


```
    digitalWrite( ledPIN, 0 );
```

```
    delay(1000);
```


```
}
```

The CIRCUIT

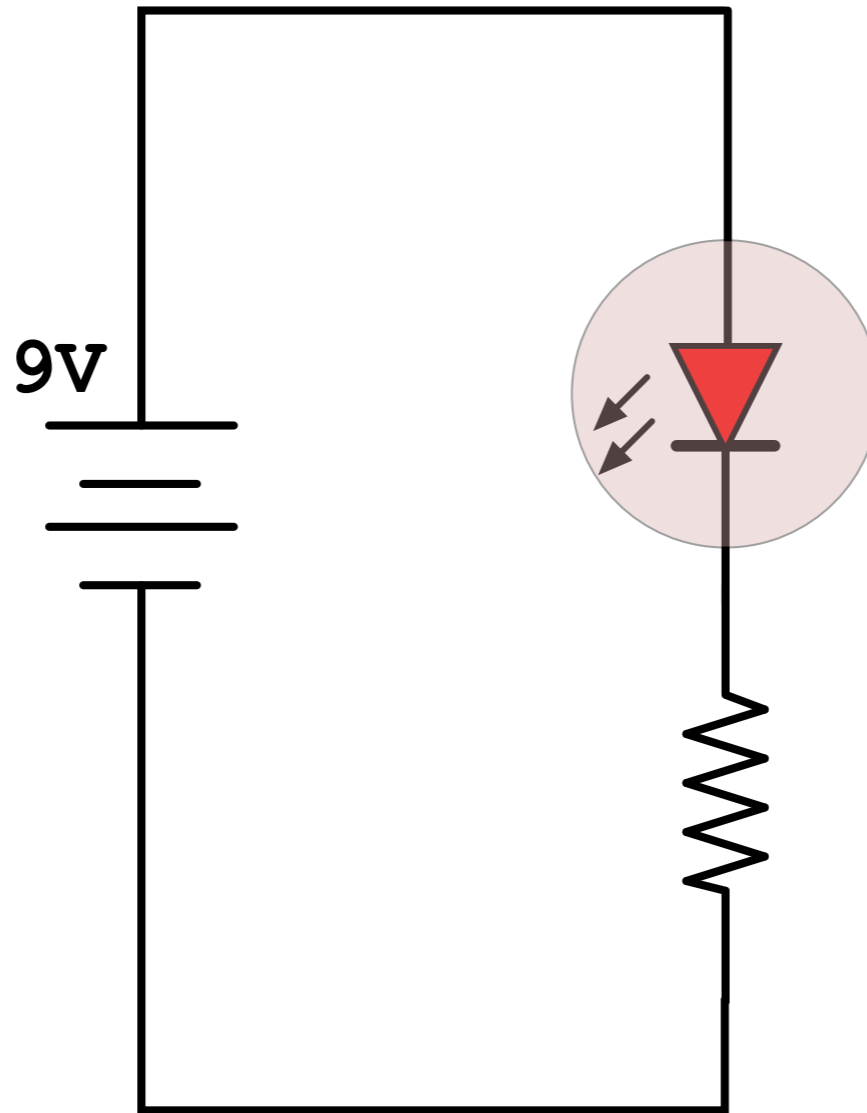
Here is the first circuit we built on a breadboard.



Let's rotate it on its side.

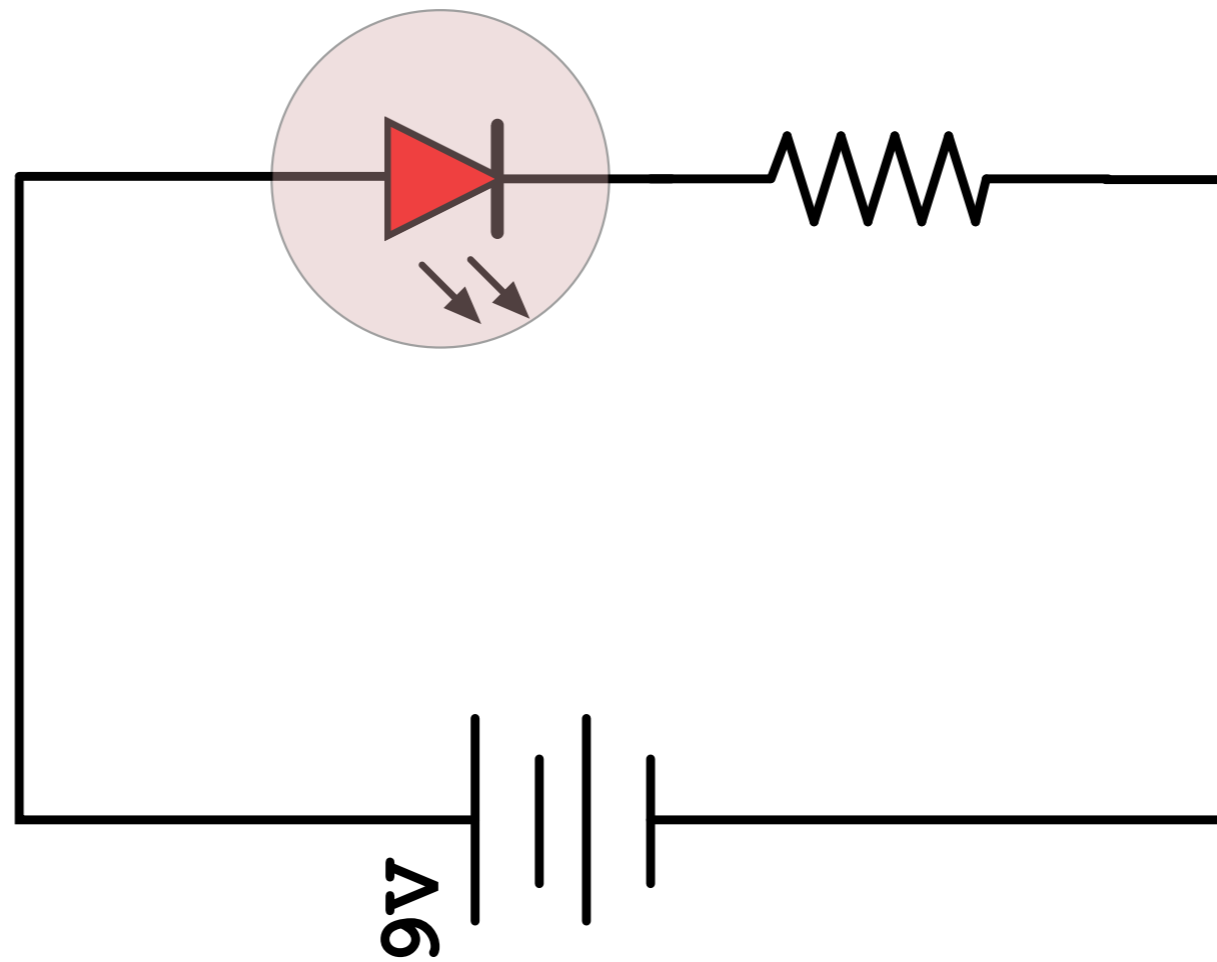


Let's rotate it on its side.

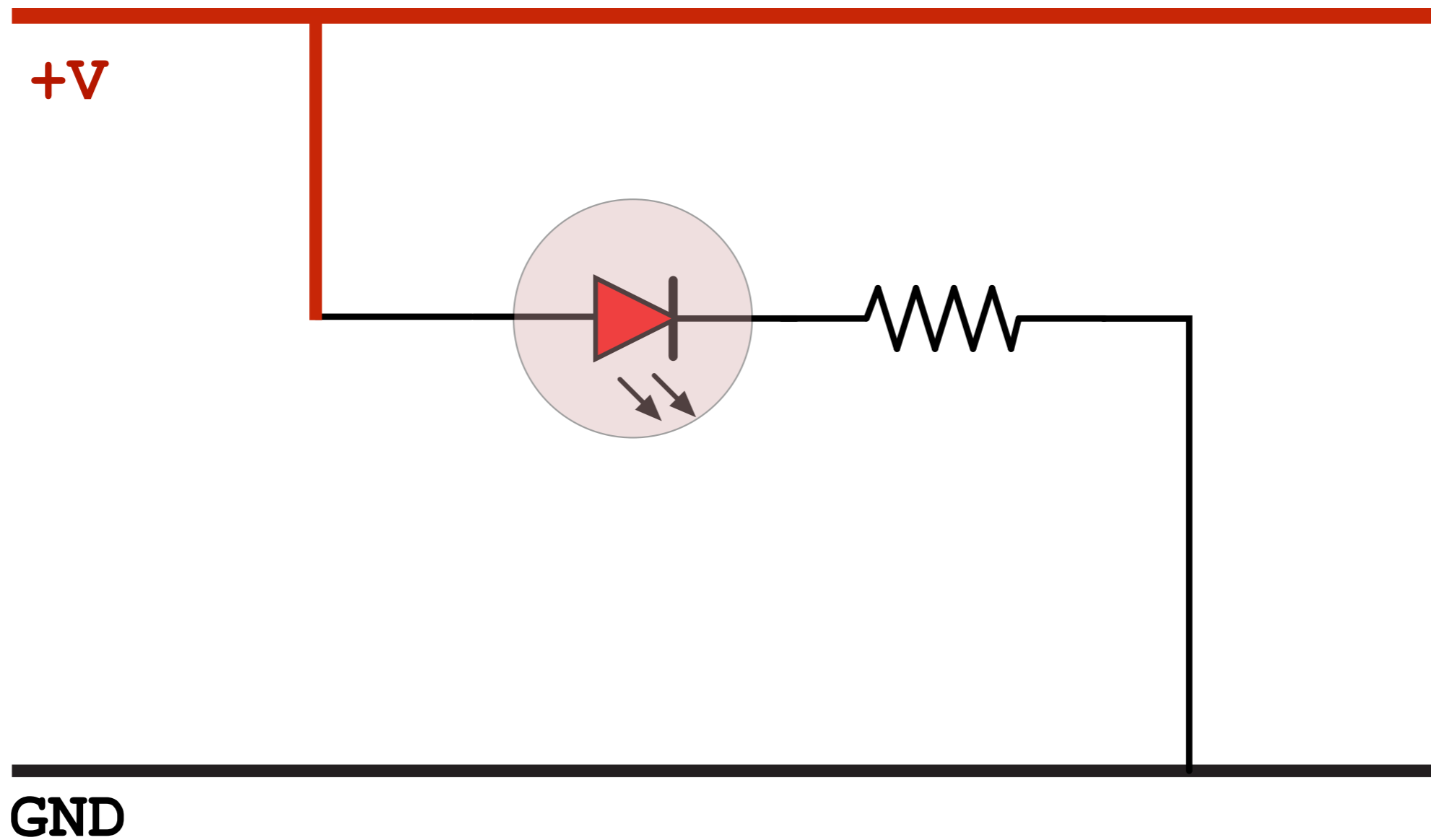

Then, remove the battery and connect to Pin 5 on your Arduino.



5V

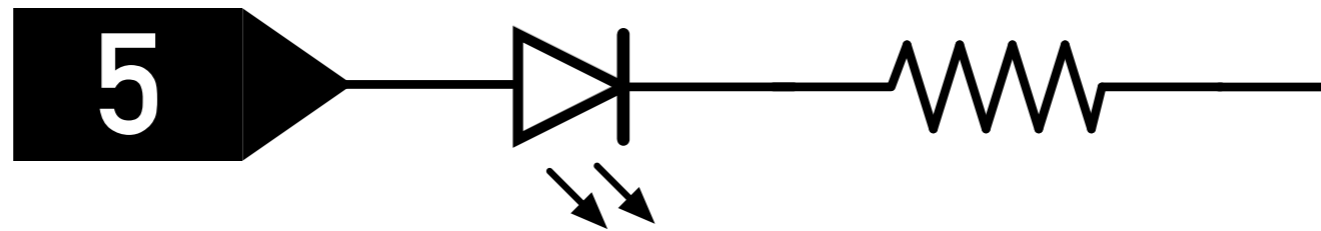


GND

Let's build.

(i turned it on its side)

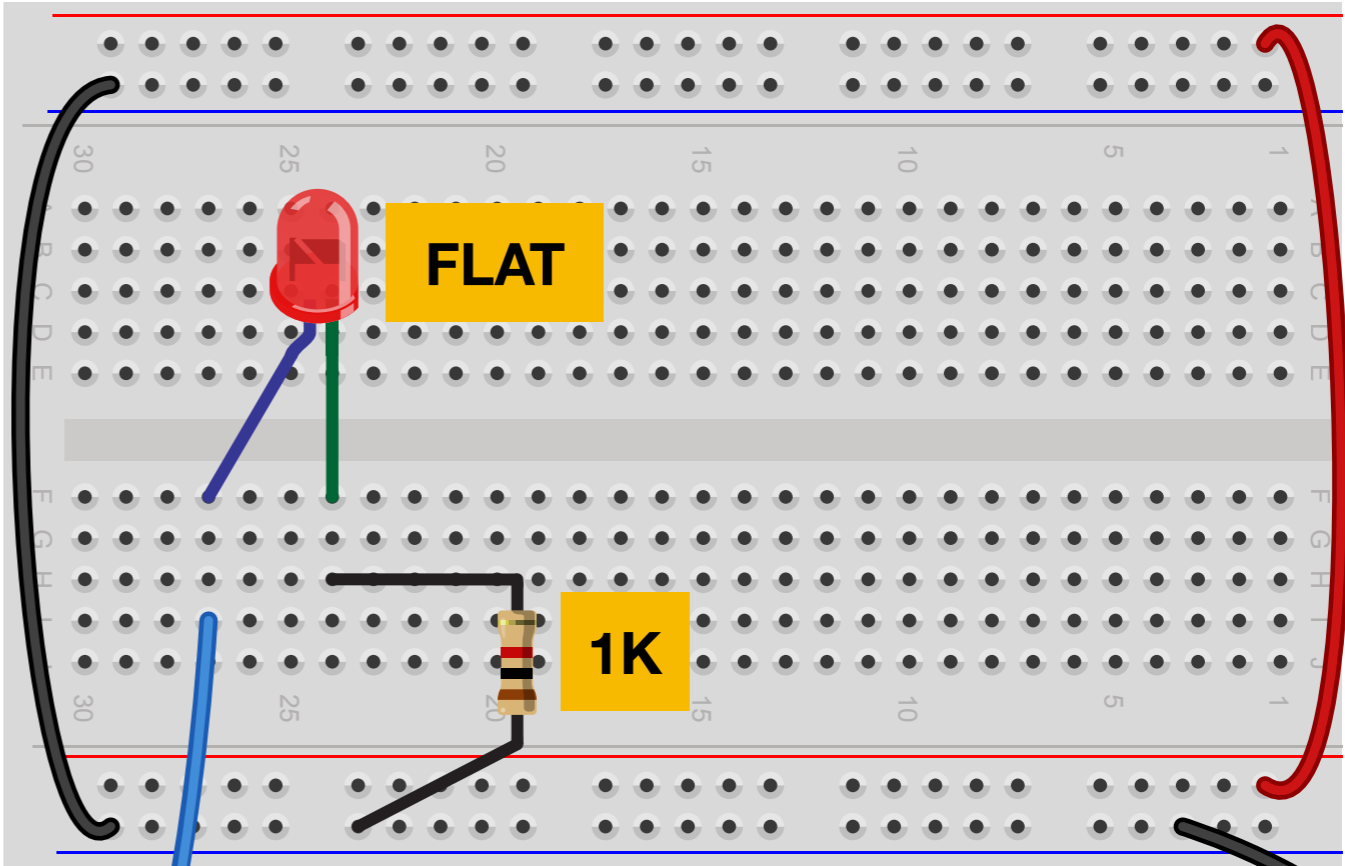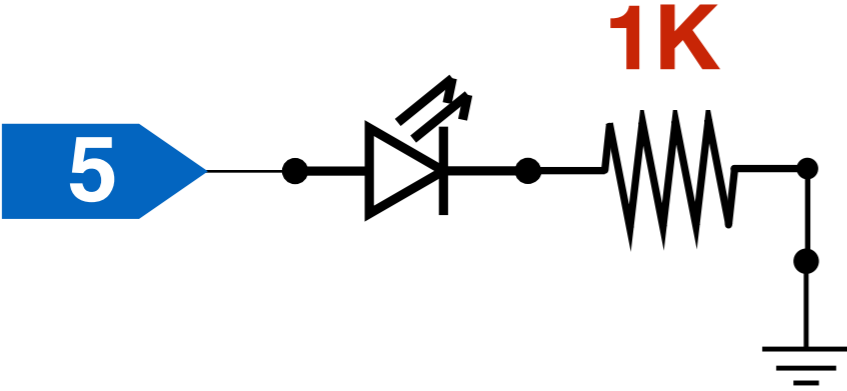


Connect a wire from:
ARD Pin 5 to LED

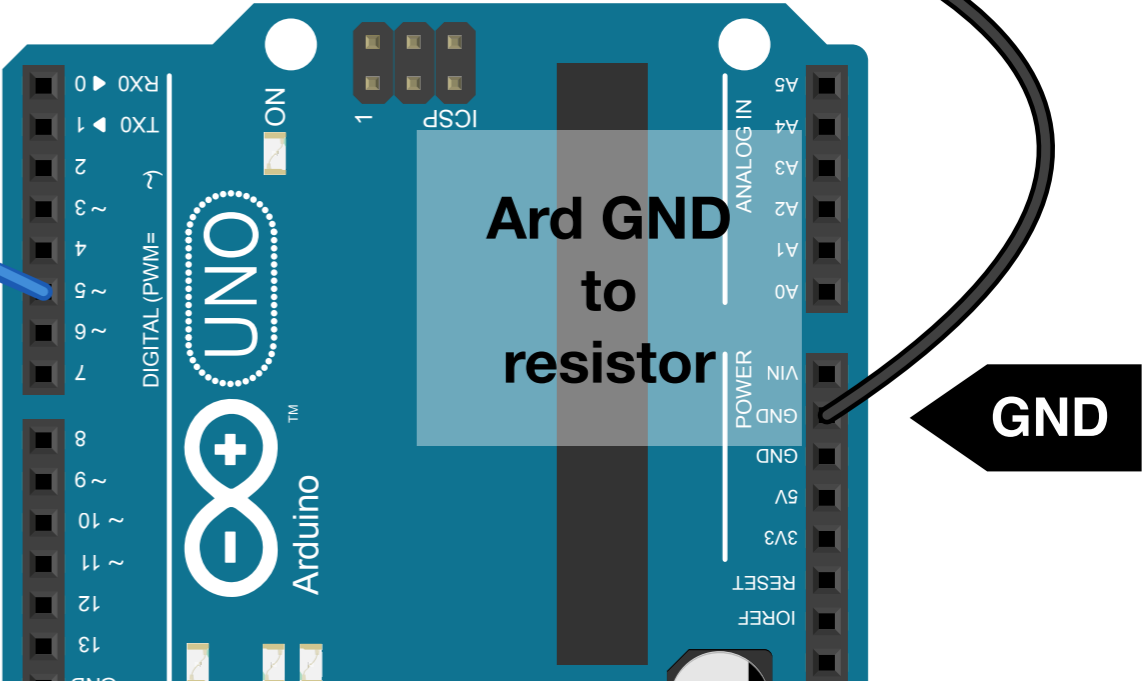

Trace the circuit. See the loop.

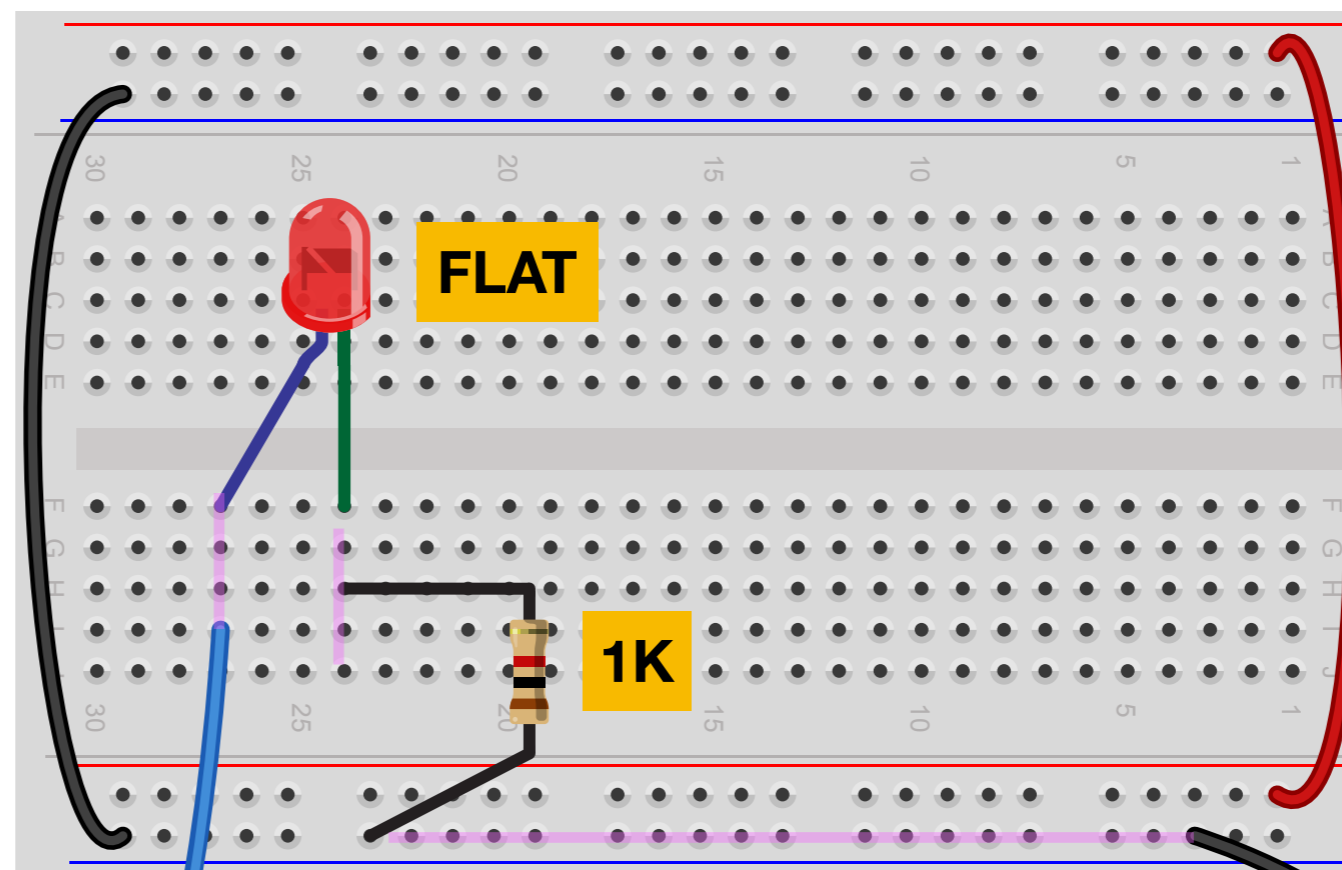Pale Pink lines
are internal BB
connections.




Connect a wire
from:
ARD Pin 5 to LED

5


Ard GND
to
resistor

GND

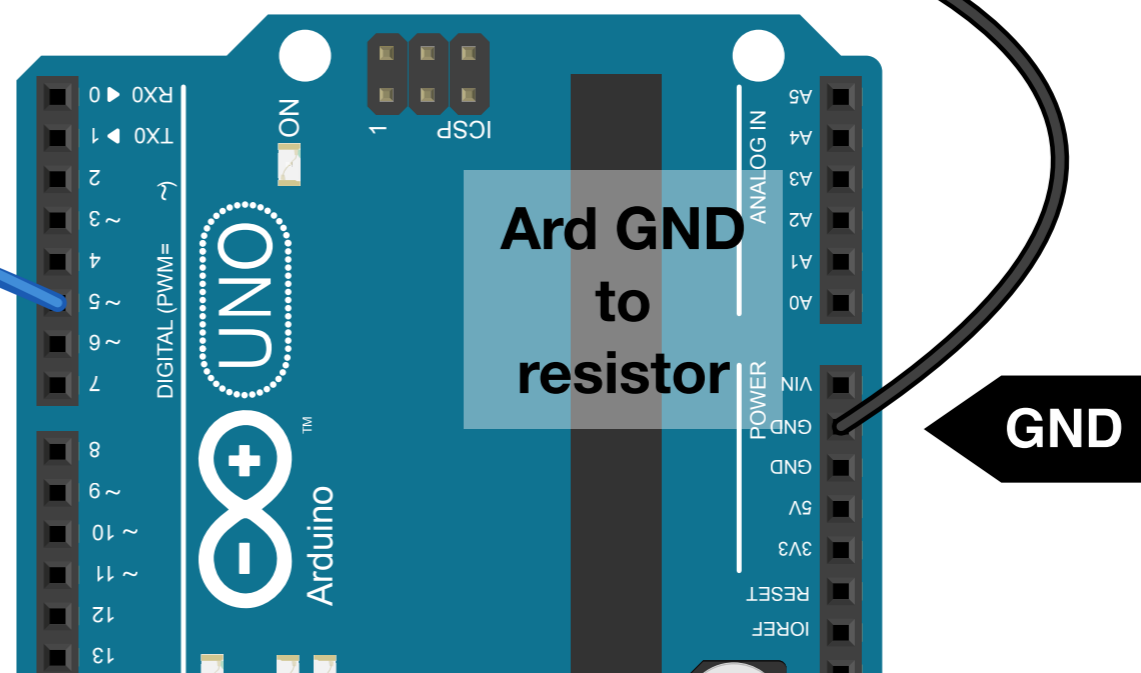


We connect to an Arduino pin, not the positive battery terminal.

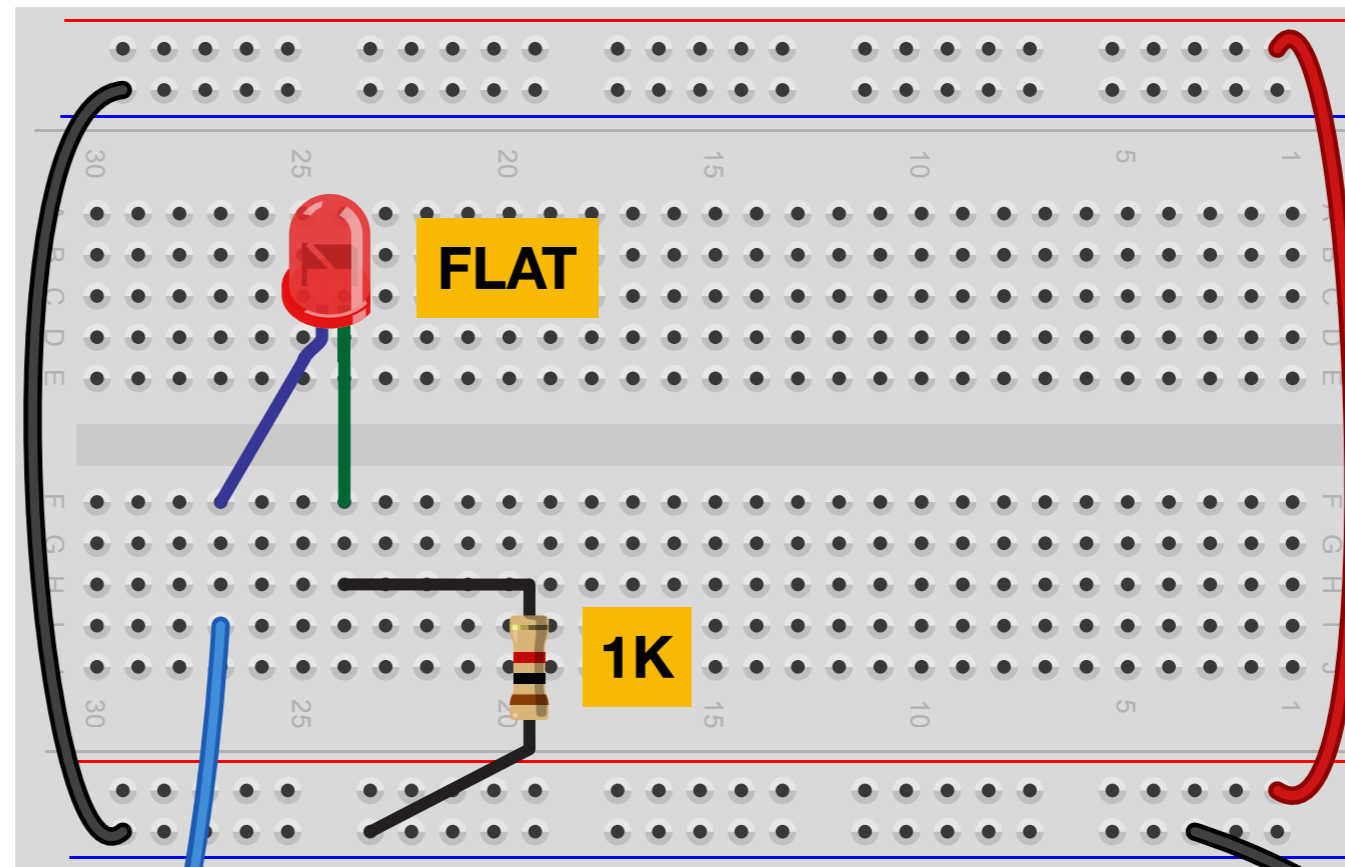NOTE:
LED round side
is connected
to Arduino pin.



Connect a wire
from:
ARD Pin 5 to LED

5

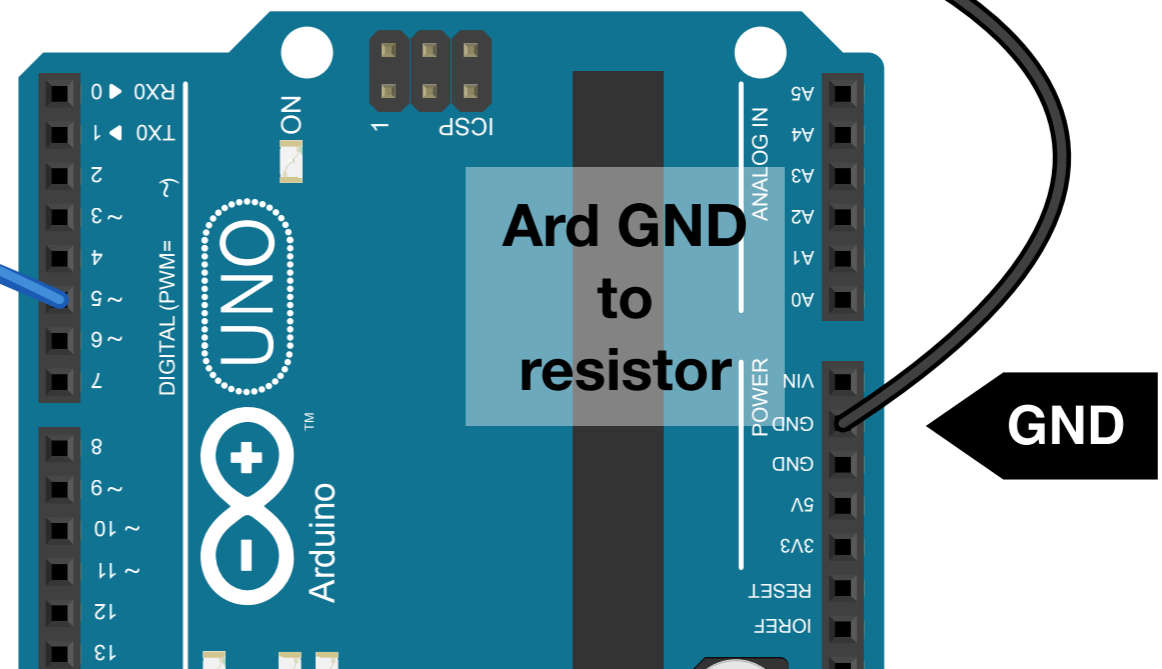


Ard GND
to
resistor

GND

Add CODE


What's Going ON ?

5V

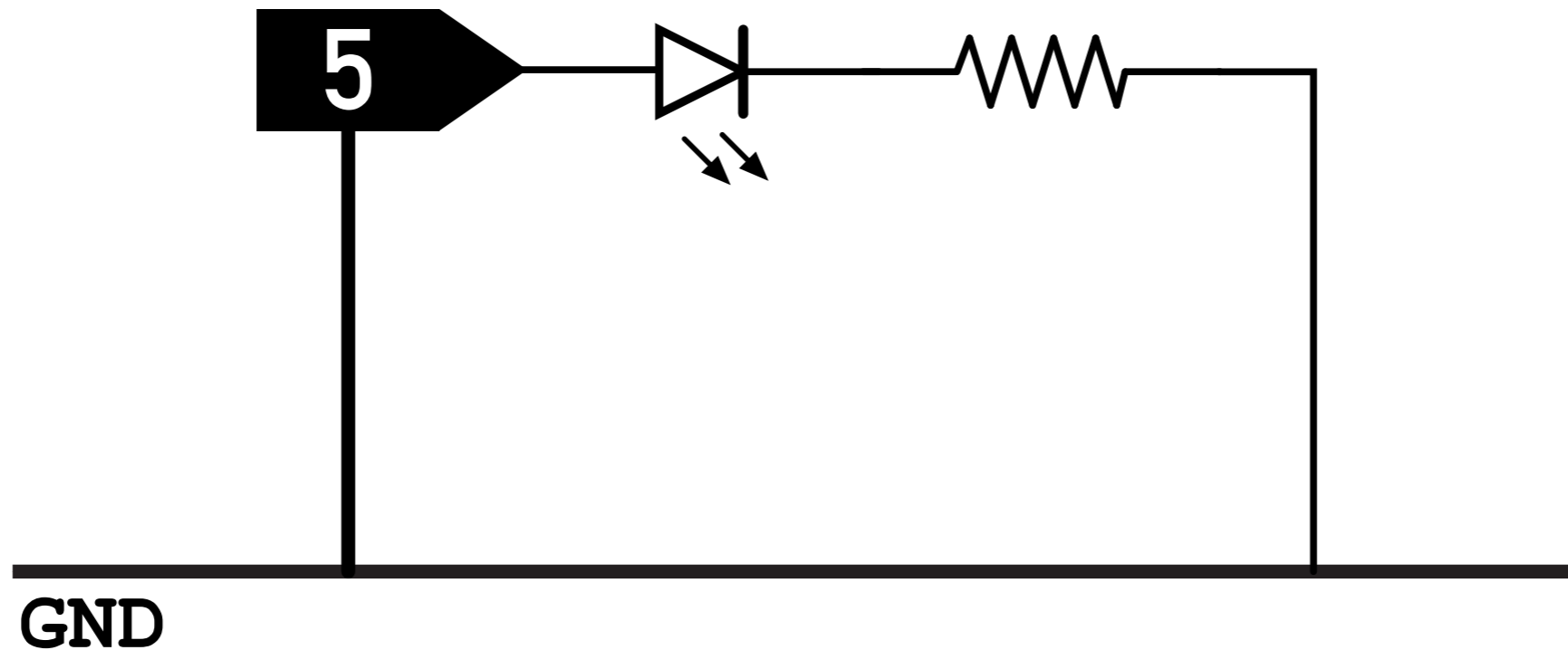

```
digitalWrite(5, LOW);
```

What's Going ON ?

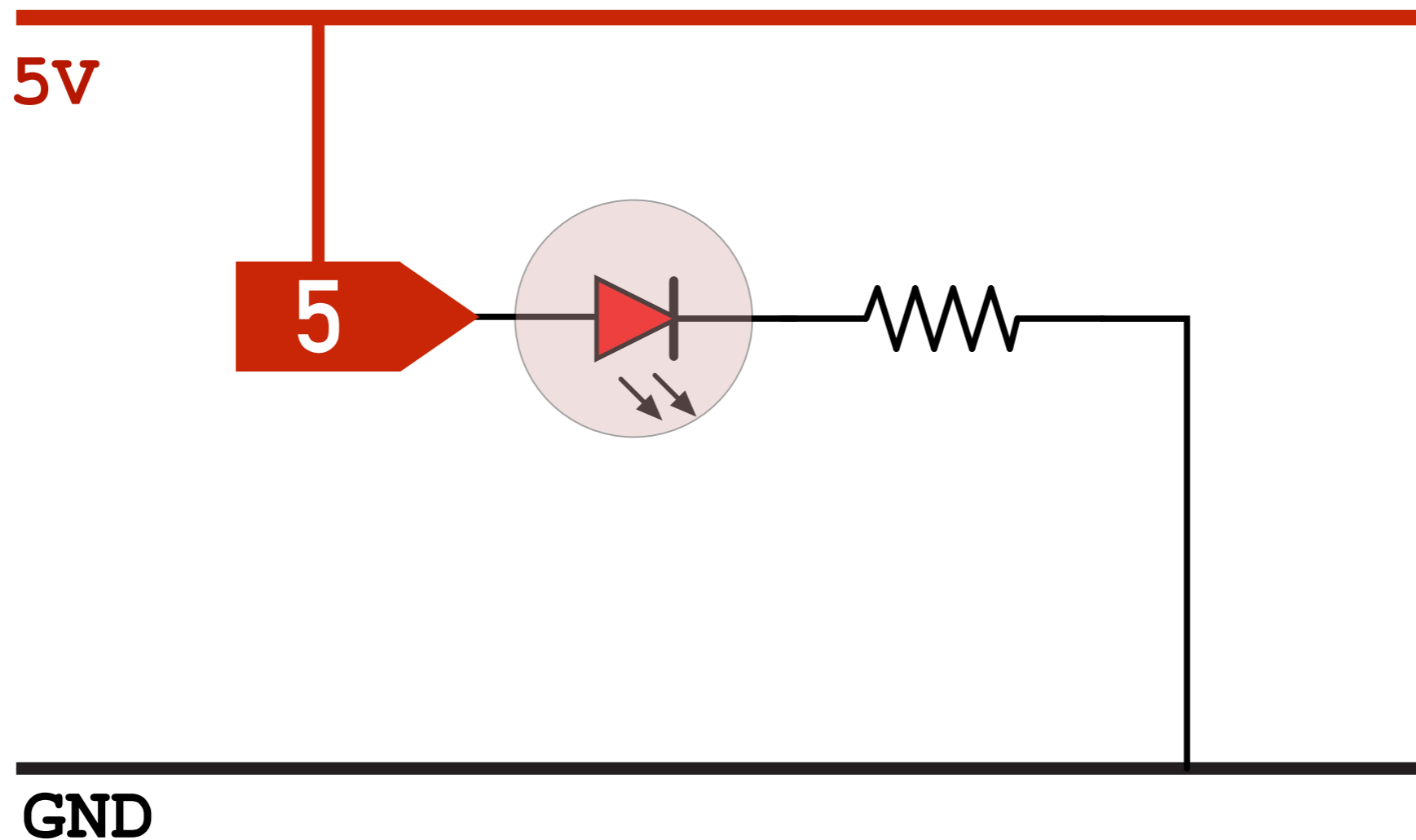


```
digitalWrite(5, HIGH);
```

RGB Variation

Can we do that with RGB?


Build it – Getting connected.

5V

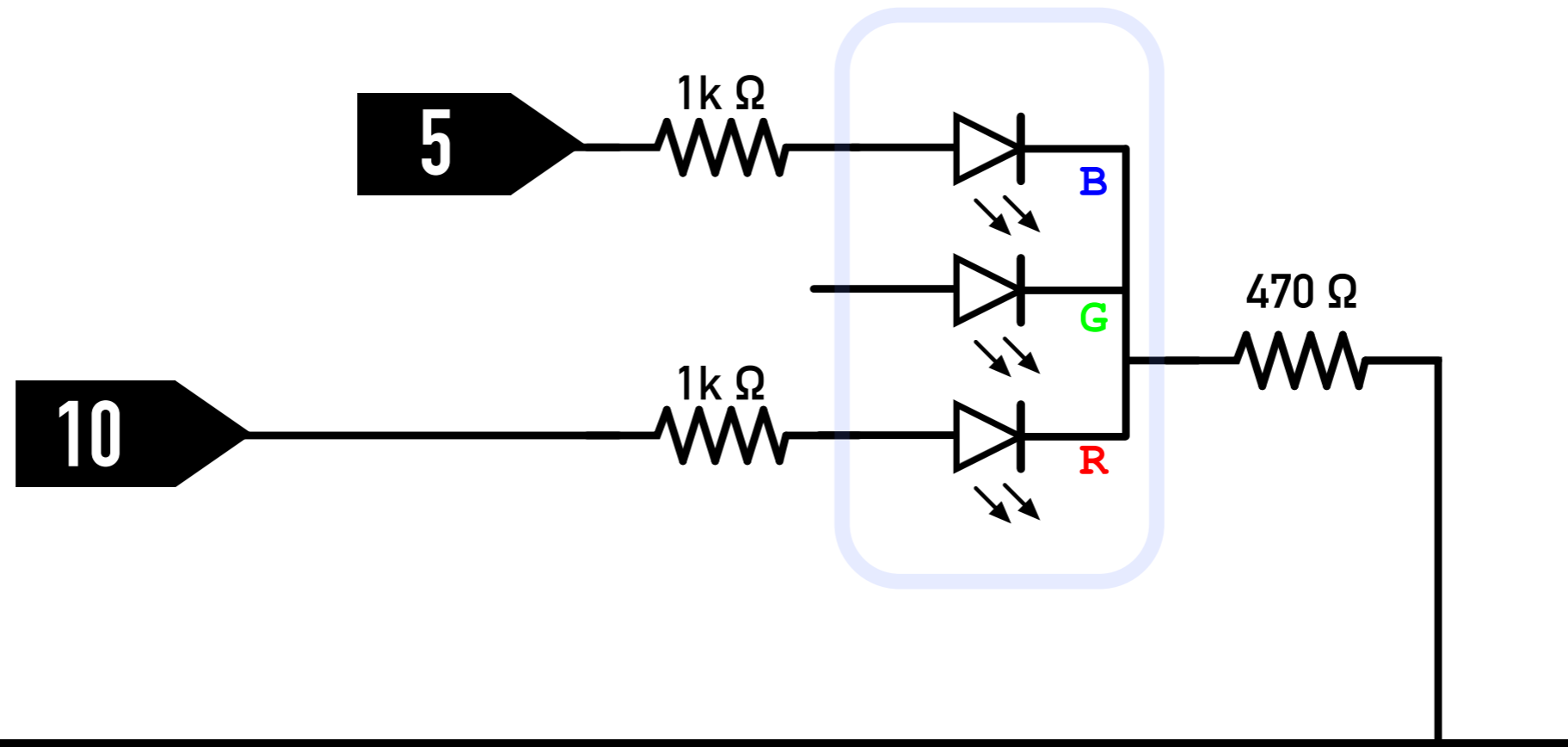


GND

Can we do that with RGB?

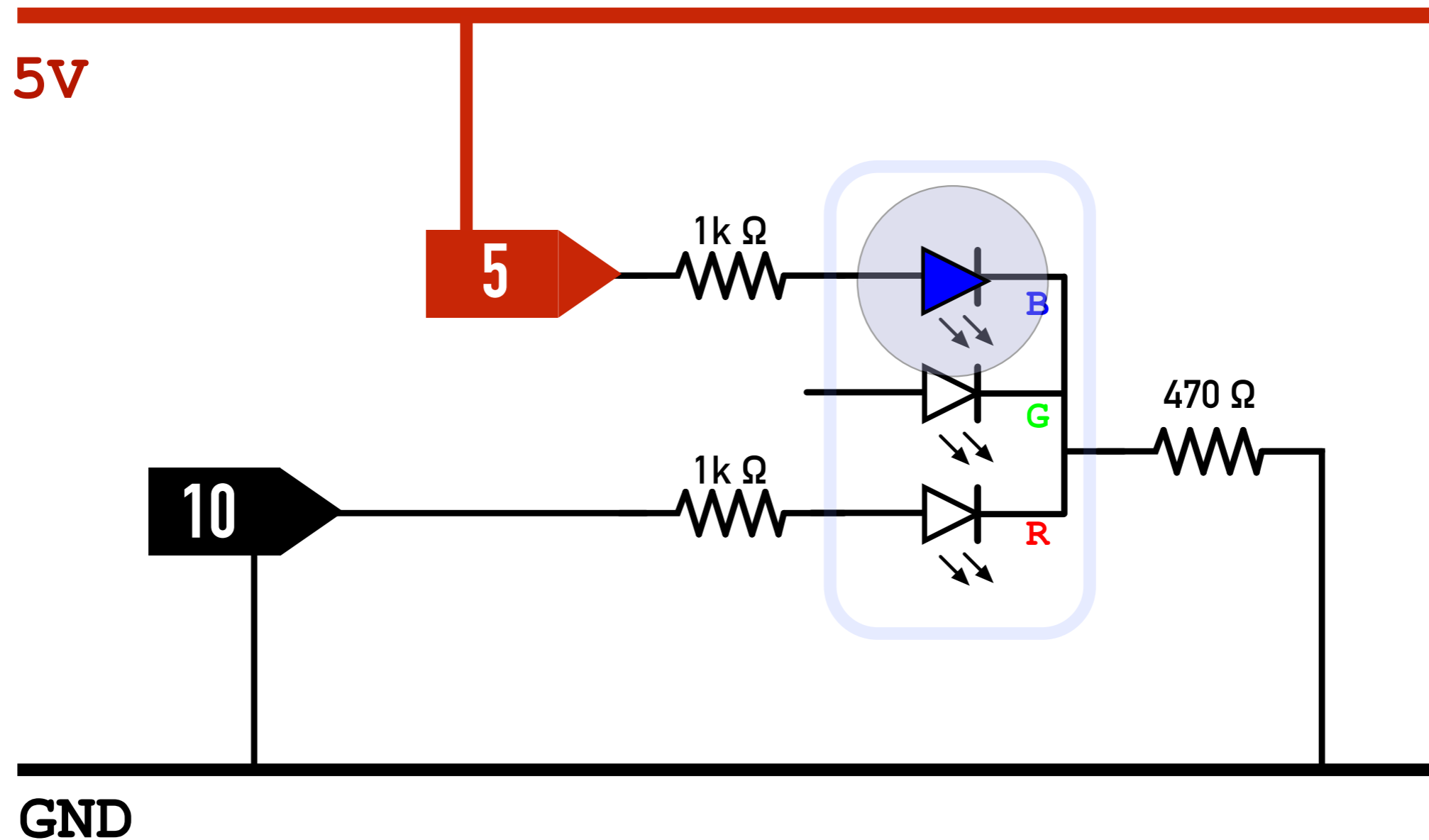

```
digitalWrite(5, HIGH);  
digitalWrite(10, LOW);
```

Can we do that with RGB?

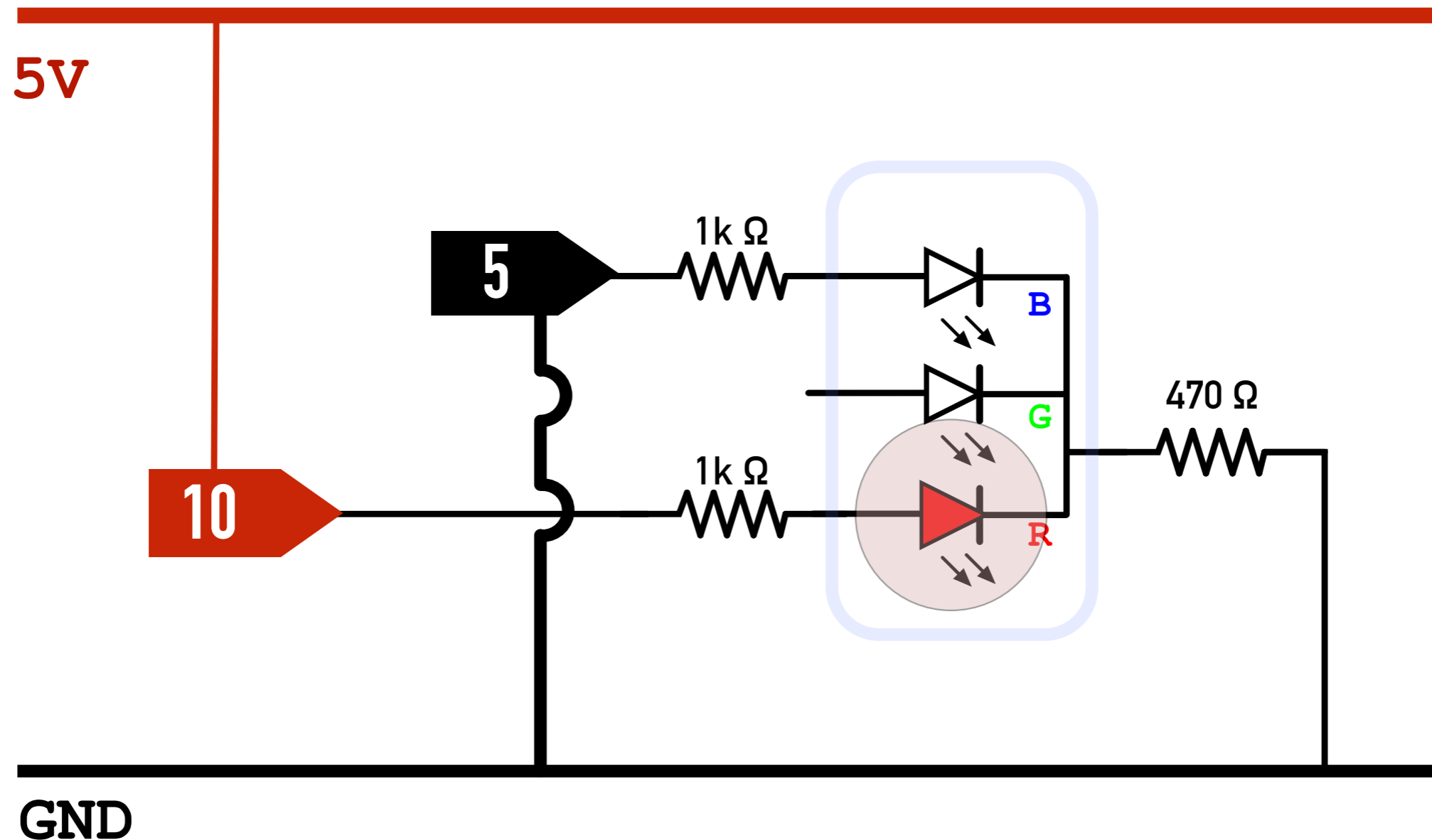

```
digitalWrite(5, LOW);  
digitalWrite(10, HIGH);
```