
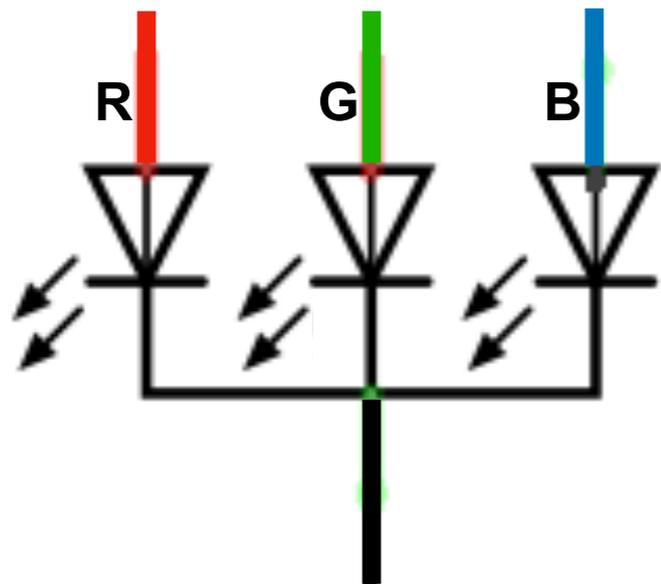


building blocks



RGB led

RGB led

New part — RGB LED

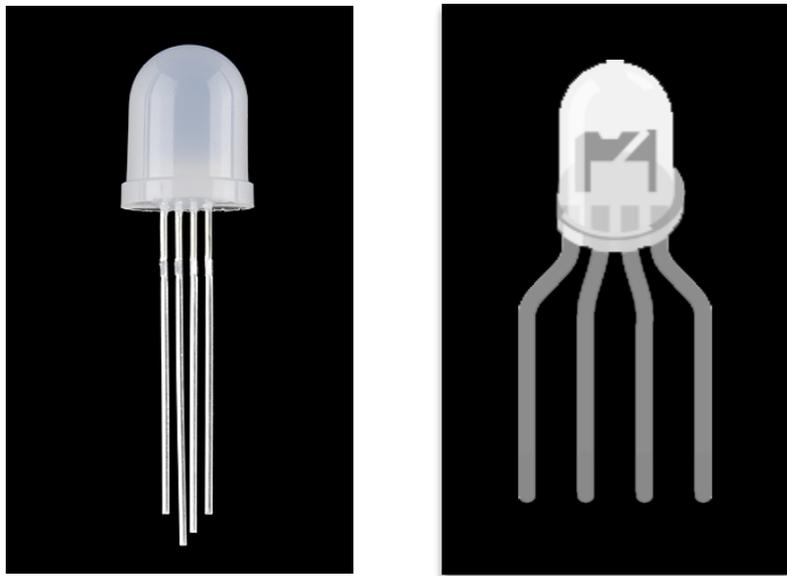

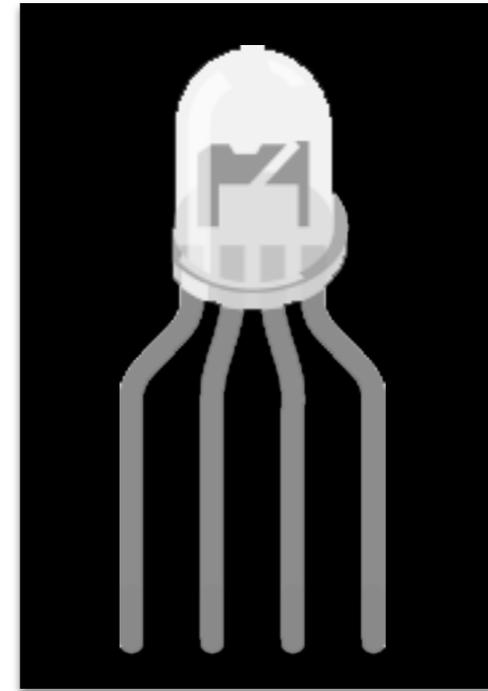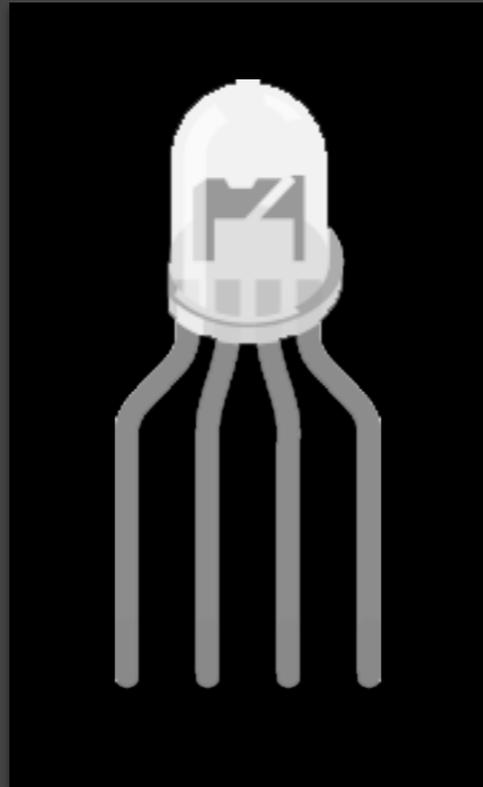
- **RGB LEDs want to GLOW (millions of colours)**
- like single cousins — they want a small amount of power — and they want it going in the right direction
- they want protection — from a current limiting resistor




RED
GND
GREEN
BLUE

**GROUND (GND)
is longest!**

New part — RGB LED

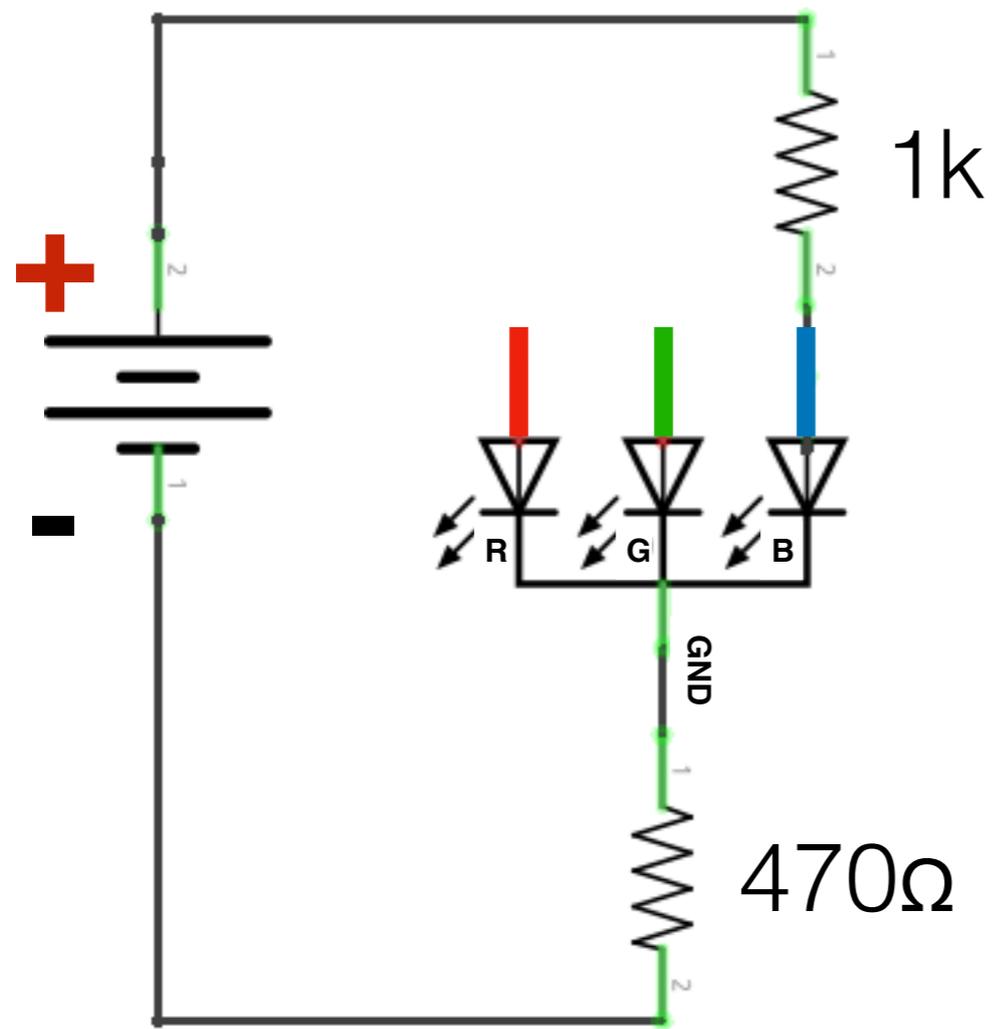

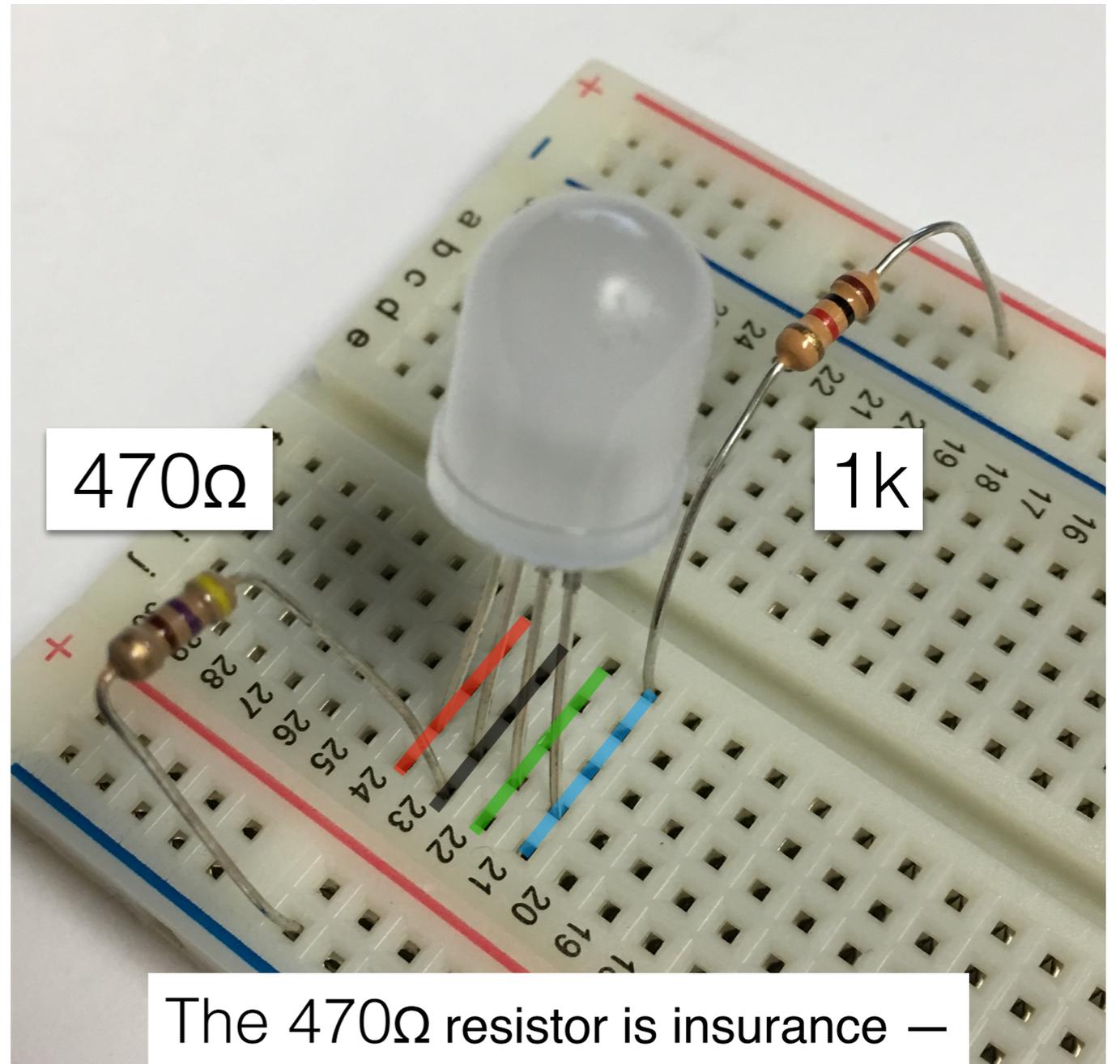
At first, put the top resistors in one at a time.




The 470Ω resistor is insurance — use it in all of these experiments!

New part — RGB

LED

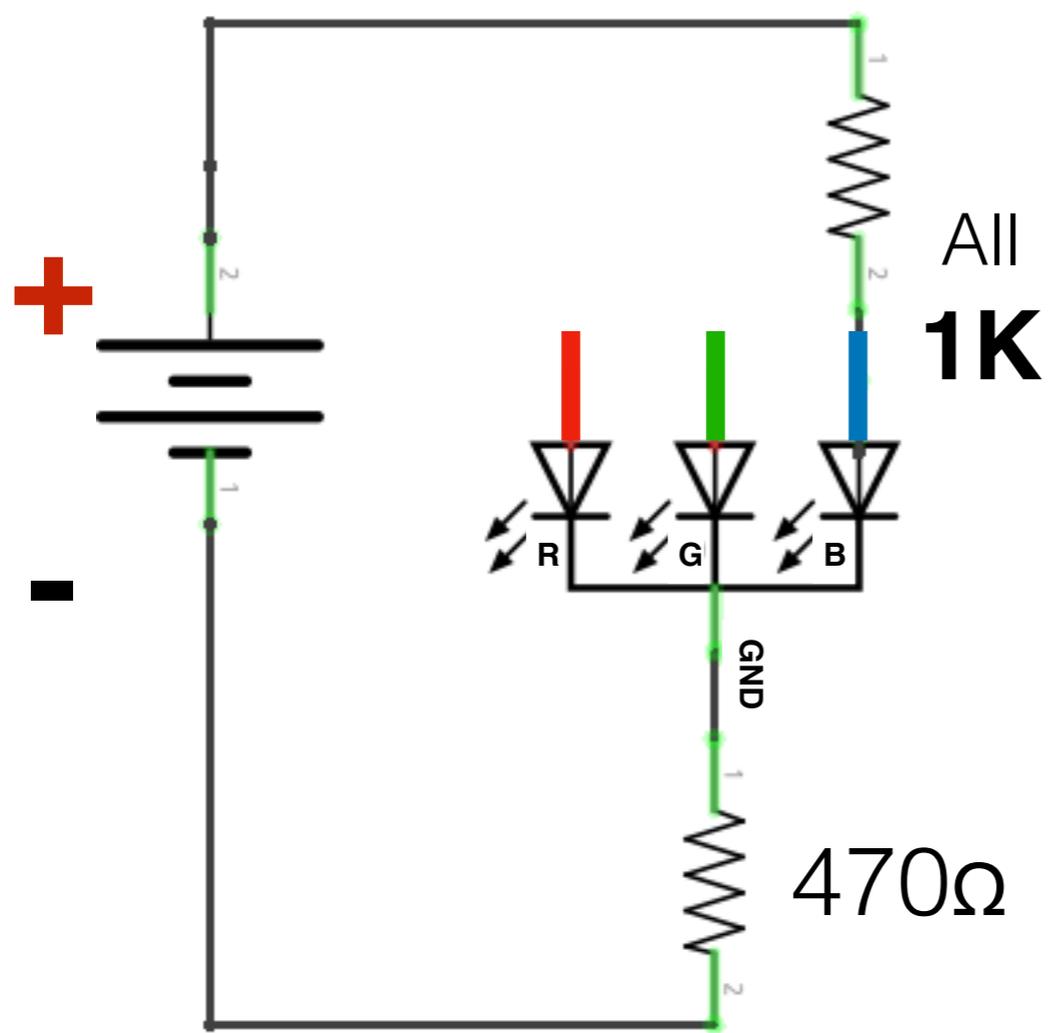

Try resistors of different value (>1k).

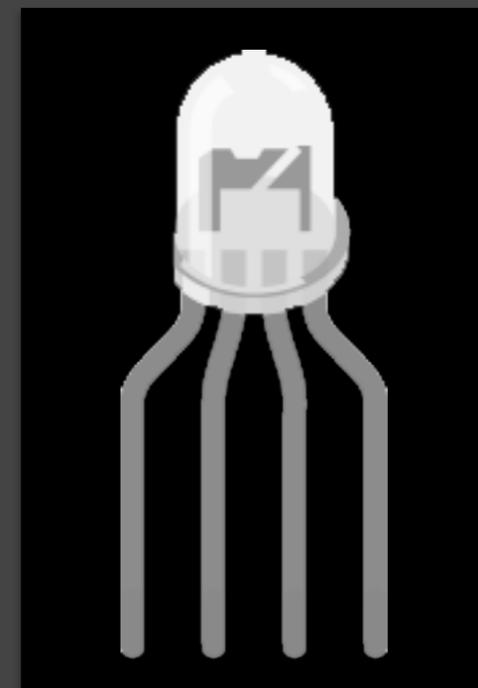


RED
GROUND
GREEN
BLUE

GROUND (GND)
is longest!

! Current Limiting Resistor !

RECALL

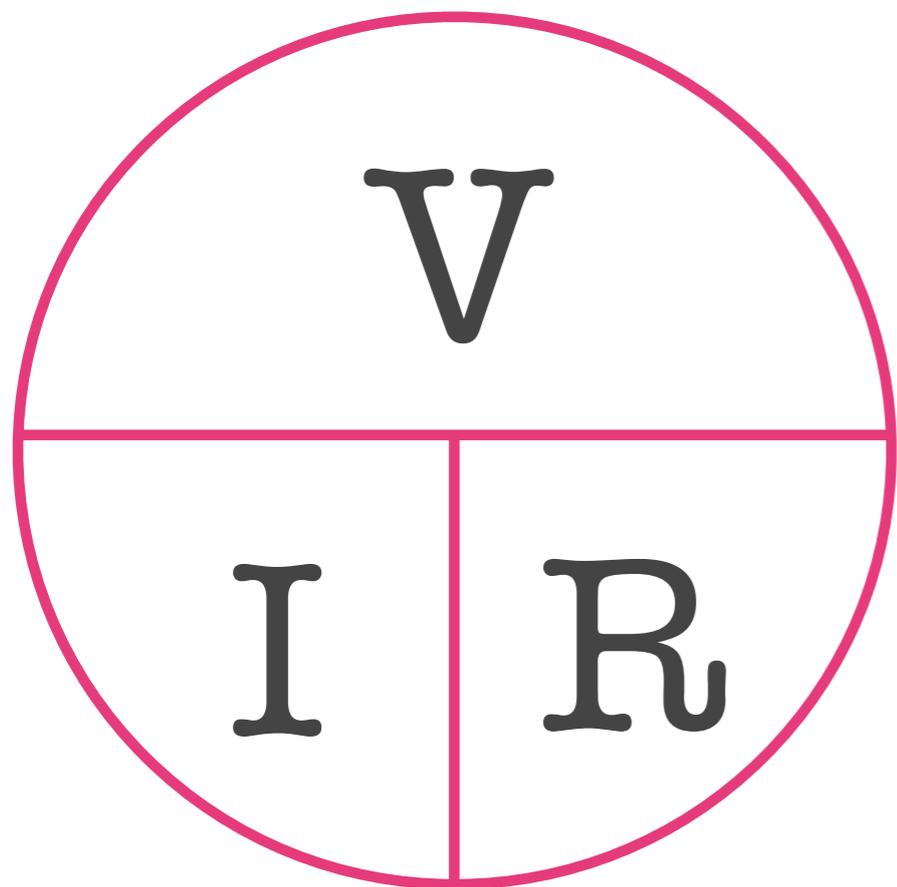


Resistors protect other components

$$I = V / R$$


This tells us that CURRENT (I) gets *smaller* as R gets bigger.

Less current = dimmer LED.

Variations - RGB -

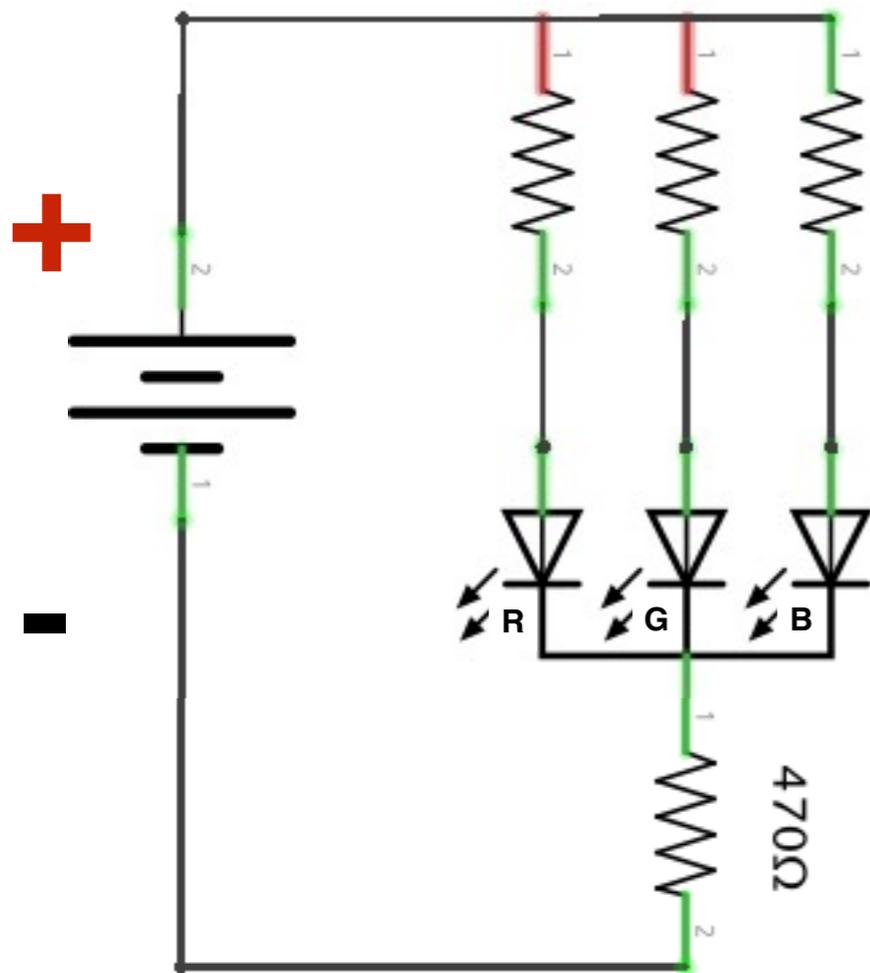

Change the size of these

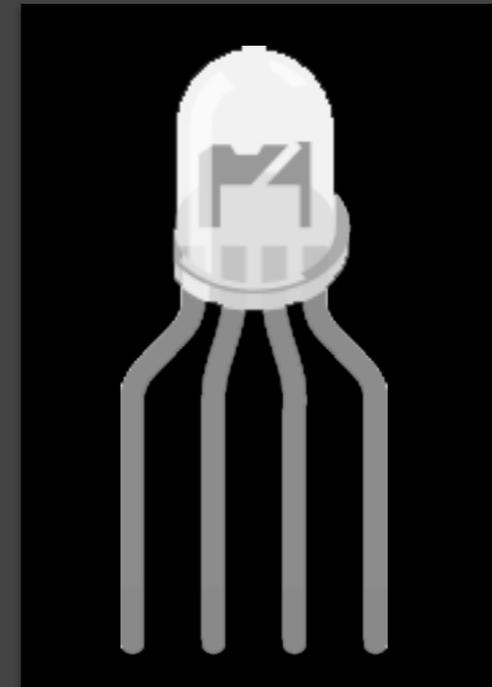

RED
GROUND
GREEN
BLUE

Try resistors of different values 100Ω - 100KΩ

GROUND (GND)
is longest!