

TERMINOLOGY

Electrons are the basic unit of electricity.

Electrons are very fast.

Electrons do NOT like to be slowed down, so they seek the path of **LEAST** resistance.

Electrons flow down hill.

Conductors

Materials that **allow** electrons to flow easily are referred to as **conductors**.

Insulators

Materials that **limit** or prevent electron flow are referred to as **insulators**.

Electrical Circuits

Are closed **loops** OR **circles** of
CONDUCTORS

Electrons (unit of electricity) **FLOW**
through **circuits** according to some basic
rules.

Electrons (unit of electricity) **FLOW**
through **circuits** according to some basic
rules.

known collectively as:

OHM'S* Law

*OHM was a guy who lived in the 1800s

OHM'S Law
describes the
relationship
between **three**
electrical
properties.

OHM'S Law describes the relationship between **three** electrical properties.

Voltage

Current

Resistance

[Find a nice intro here.](#)

OHM'S Law says:

$$V = I \times R$$

Read as :: **V** equals **I** times **R**

or :: **Volts** equals **Current** times **Resistance**

Voltage

The difference in electrical potential (energy) between two points in a circuit.

Measured in Volts (v)

THINK: Amount of **force** of **electrons**.

Current

A measure of the **quantity of flow** of electrons

- Unit is Amps or Amperes (A)
- Often measured in milliAmps (mA) or thousandths of amps

THINK: current (flow) of a river.

Resistance

- Measured in Ohms (Ω)

A measure of the **restriction (opposition)** to the **flow** of electrons in a circuit. (Note :: all conductors have a resistance, weird - its just small).


THINK: Tap or damn blocking flow of a river.

Electrical Components have
VOLTAGE and **CURRENT**
limits.

If we fail to respect these
limits we can **hurt** our
components.

This can involve smoke and heat.

OHM'S Law

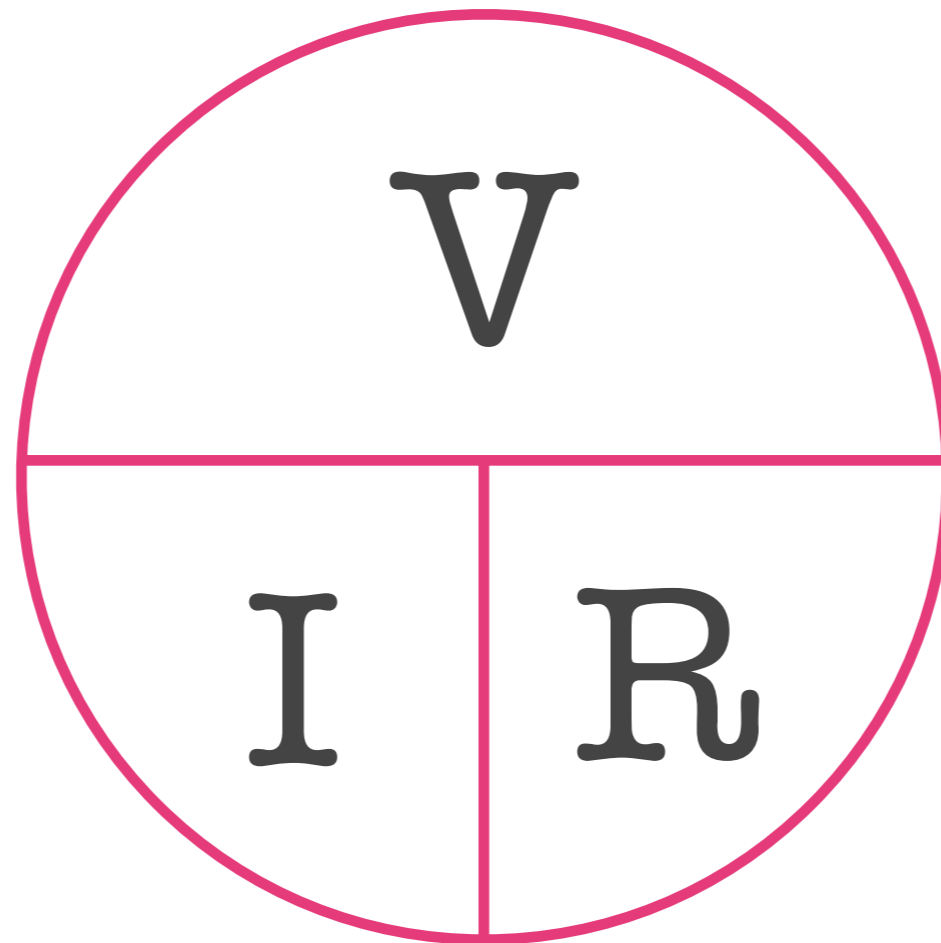

So, our **GOAL** when we make our first circuits will be to create loops of conductors that let electrons flow.

Just like an

So, our **GOAL** when we make our first circuits will be to create loops of conductors that let electrons flow.

Just like an

ESCHER

ESCHER's

Waterfall (1961) is an excellent way to visualize what happens inside a circuit.



Image is cropped — source.

Continuous loop.

V = height of fall

I = amount of water

R = barriers on path

It also captures the impossibility of what we are doing.



Image is cropped — source.