

TRANSISTORS

building blocks




Part 1

Transistors

What are Transistors?

Transistors

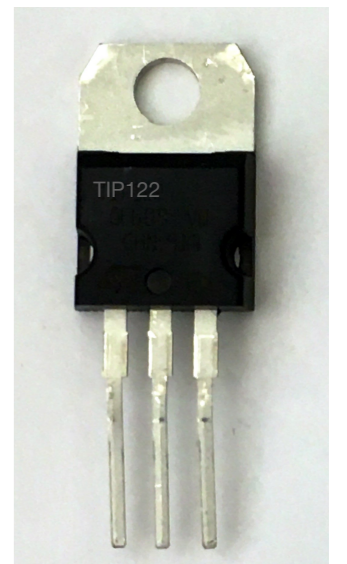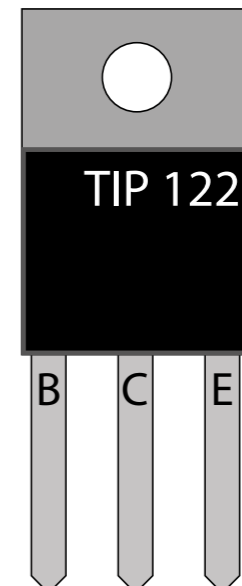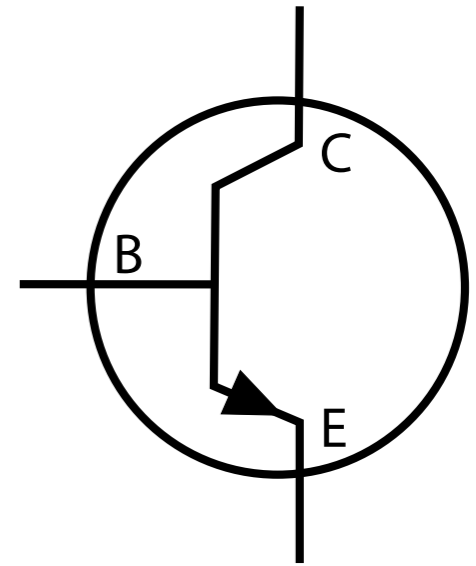Electrical
switches we can
control with a
signal from
Arduino




Know your TO-220

These components have the same packaging, called TO_220.

But they are not the same.

The component on the left is a **TIP122 transistor**.




On the right, 7805 voltage regulator.

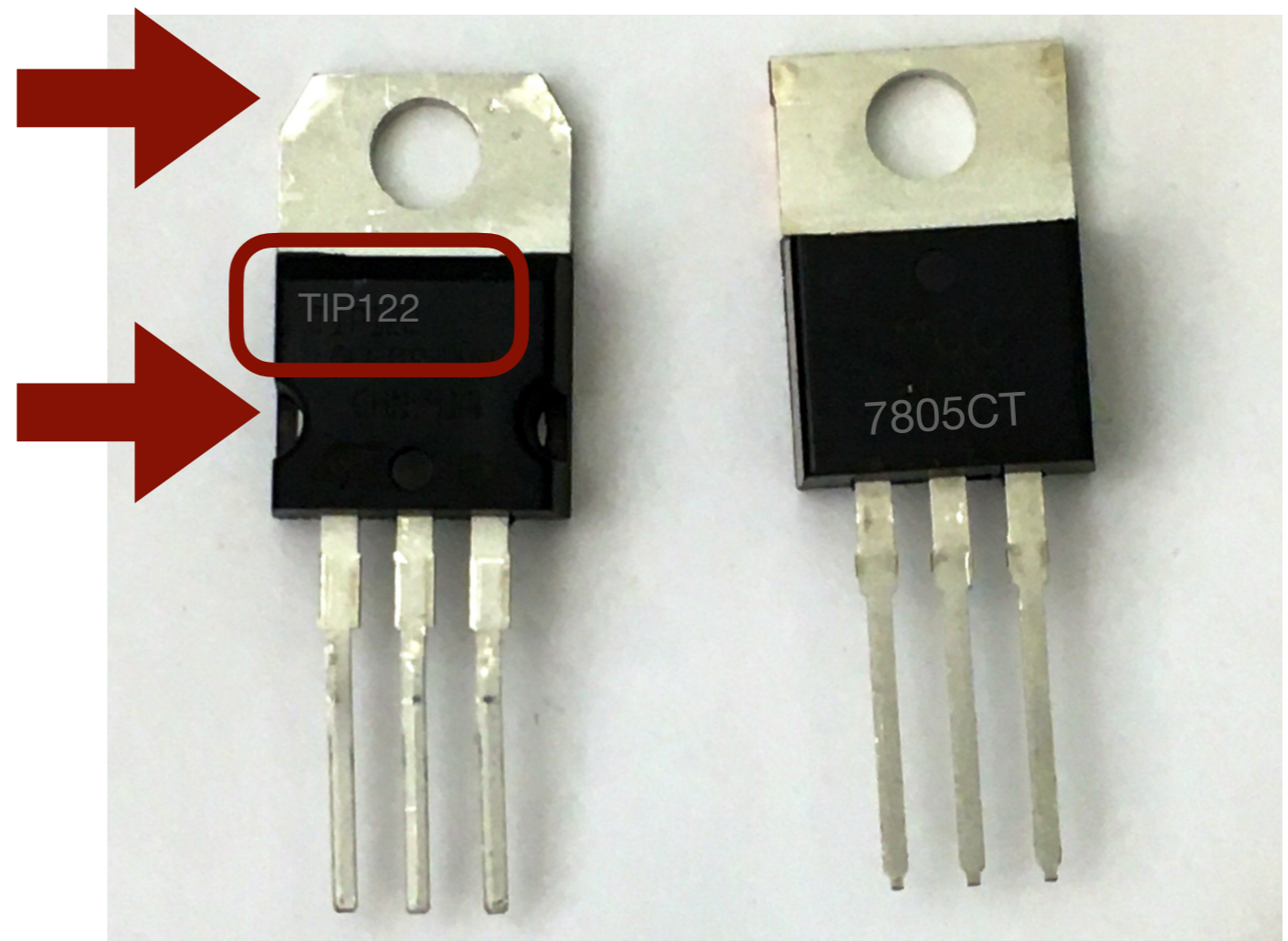


TIP122


7805

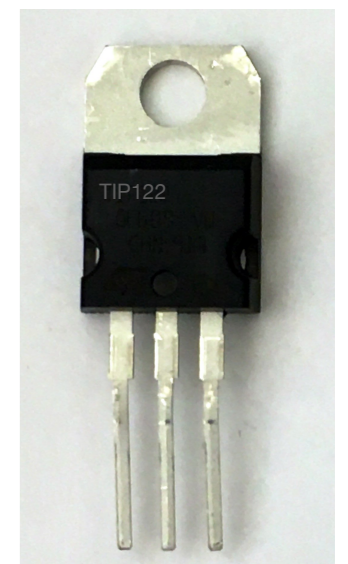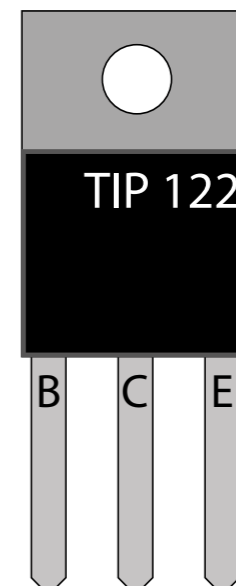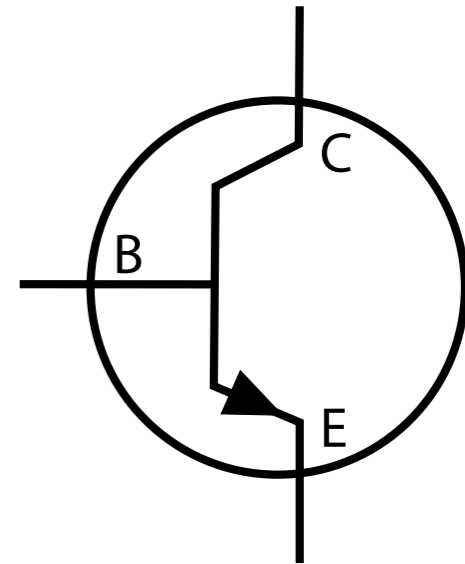
- There are two main types of transistor, NPN and PNP.
- We have **TIP122** NPN transistors in our kits.
- NPN transistors are connected to the negative side of the circuit they switch.
- NPN turn ON with a positive signal (HIGH, 1)
- Identify the legs.
 - B**= Base
 - C**= Collector
 - E**= Emitter



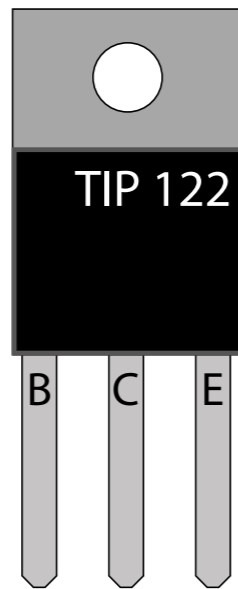




B= Base
C= Collector
E= Emitter

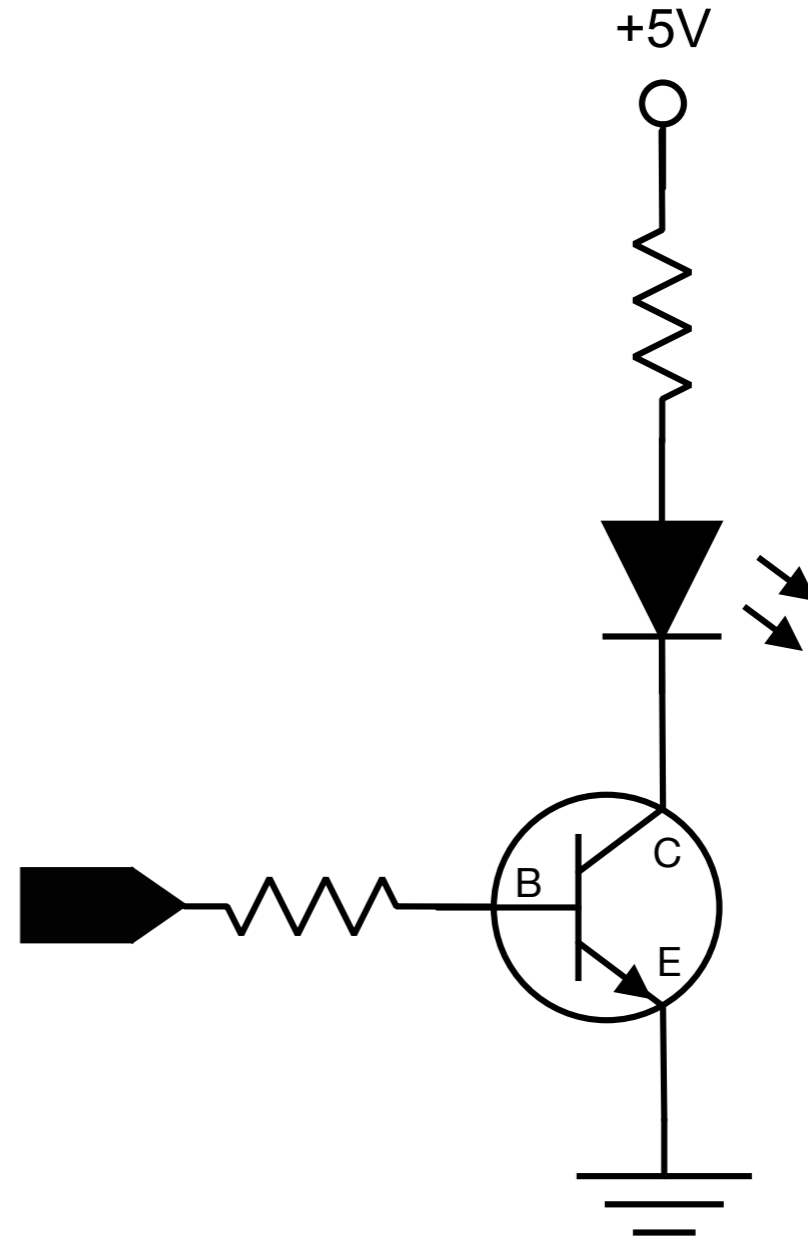

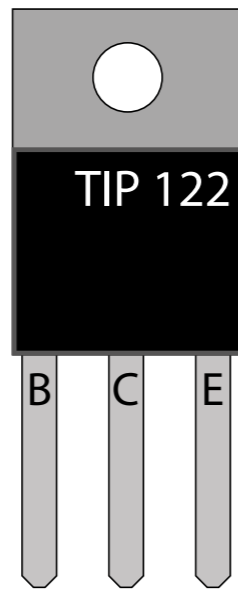

B= Base
C= Collector
E= Emitter

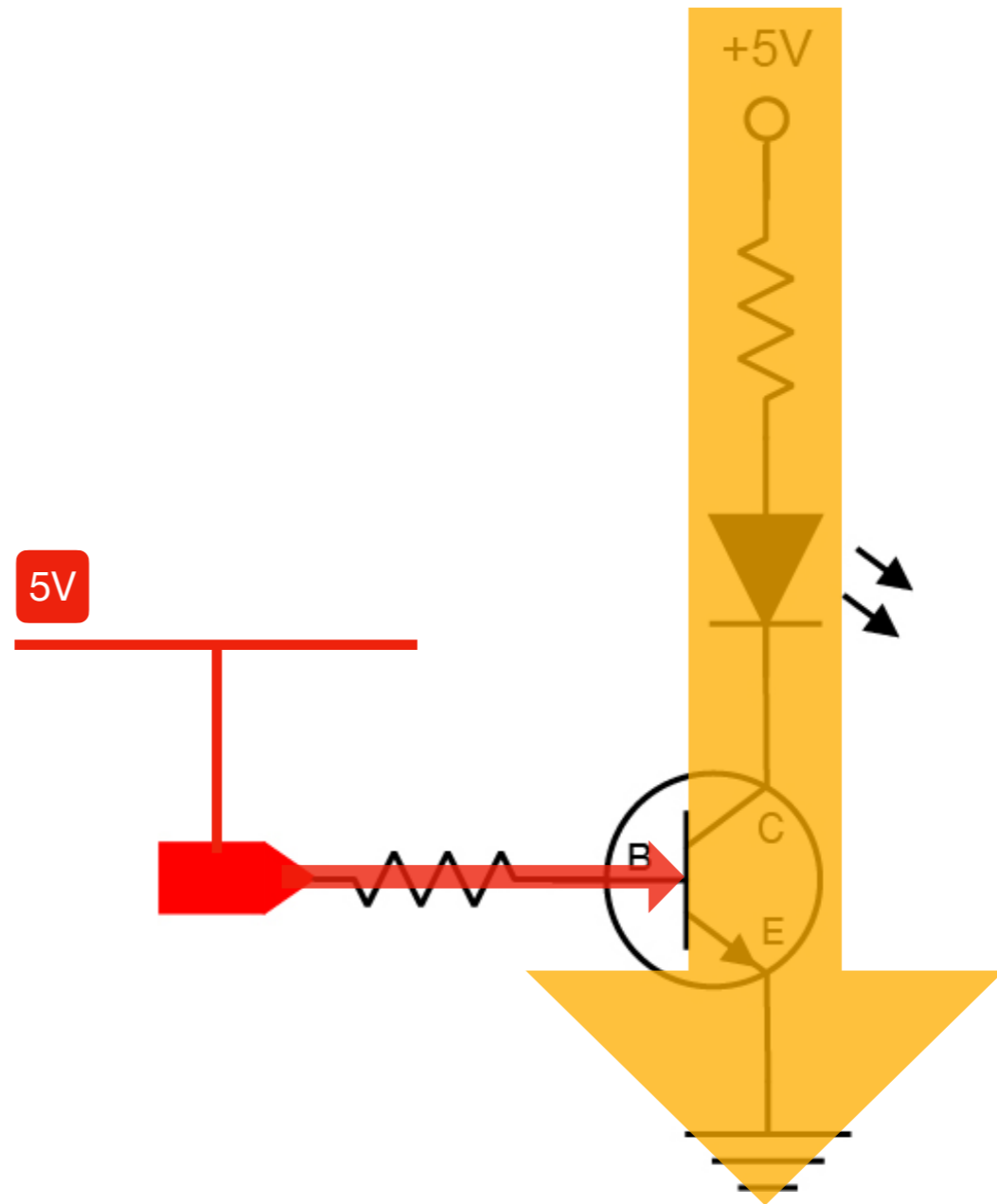

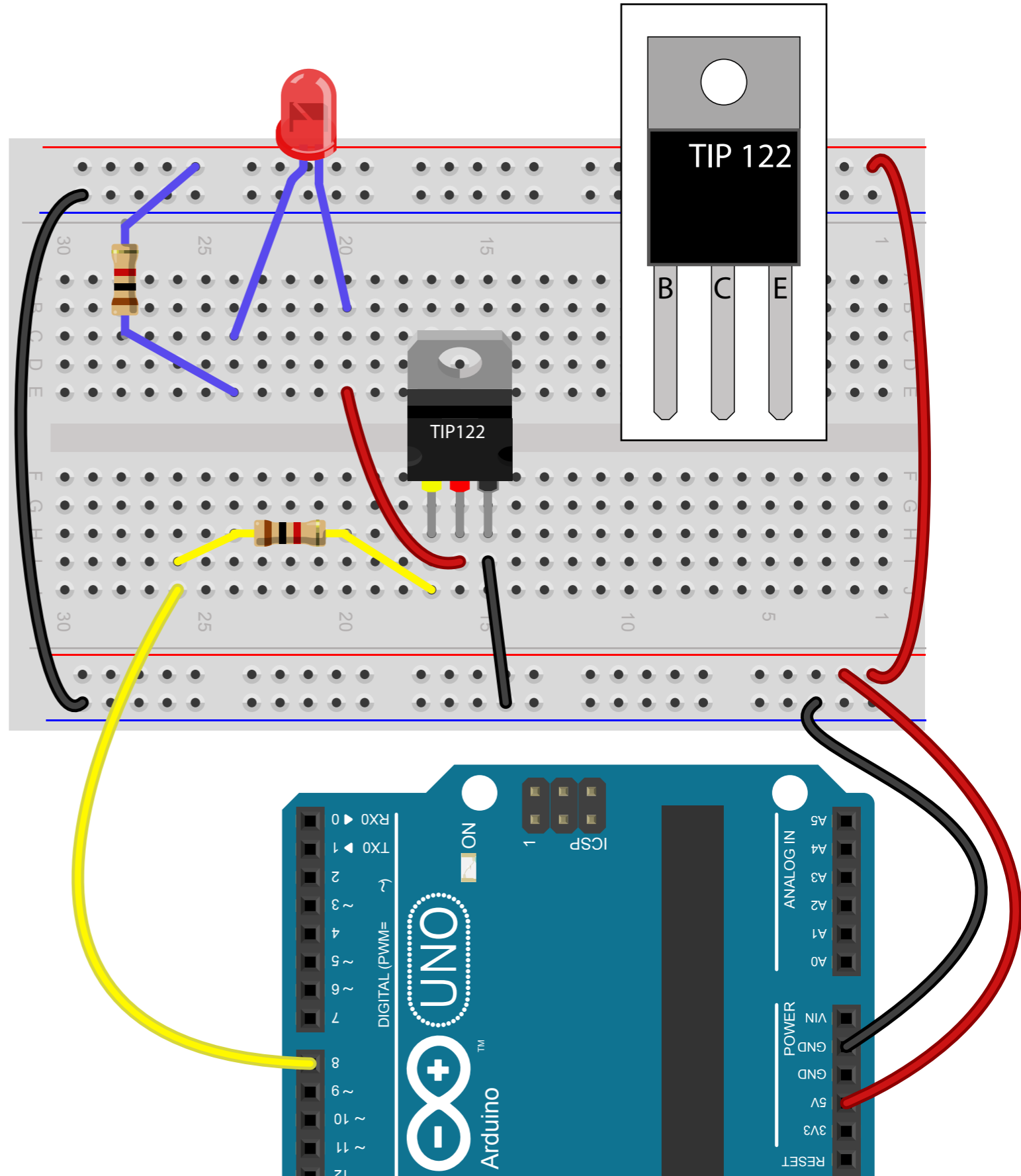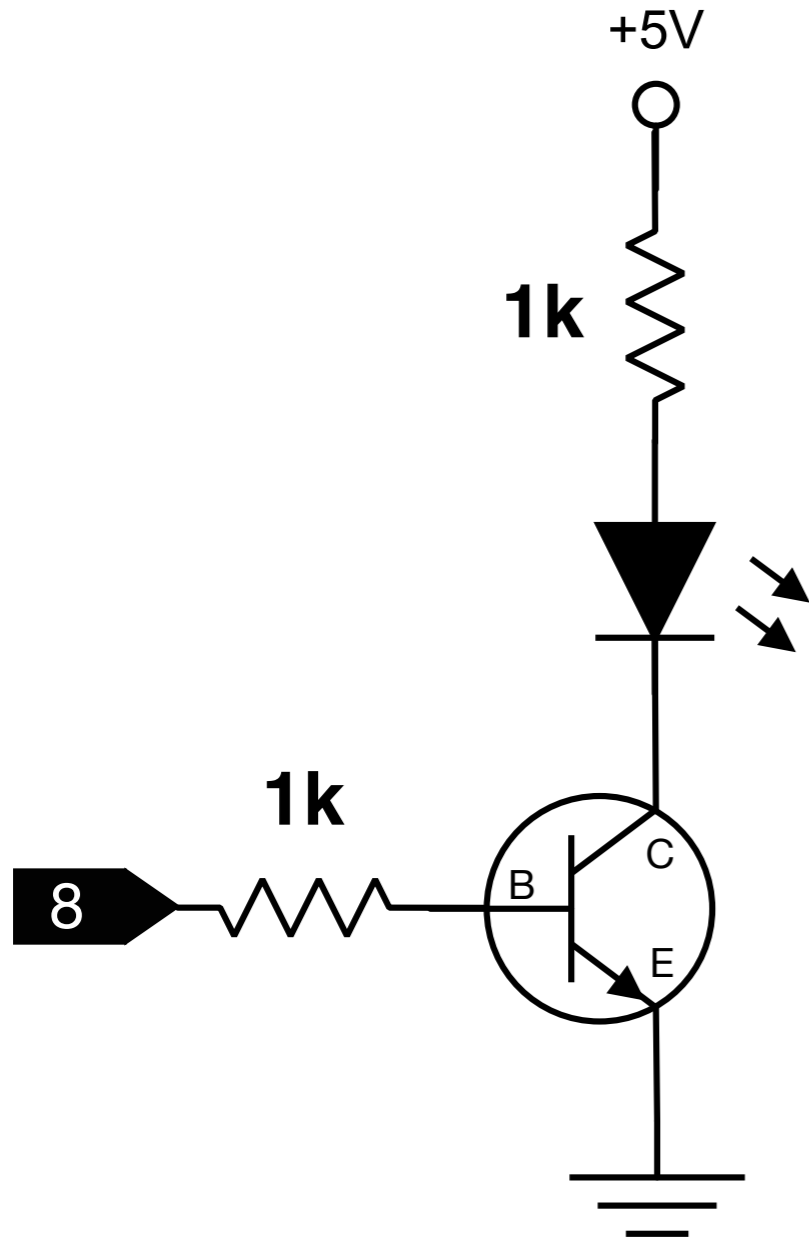


MAX current of parts in our kit

SOURCE (mA)



Tip122

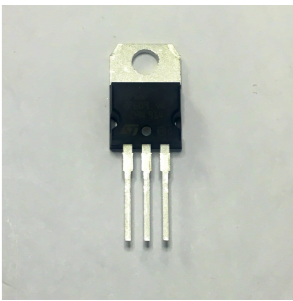

20mA

40mA


60mA

200mA


1000mA

>1A


5A

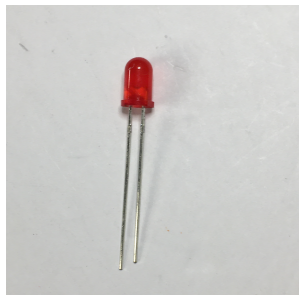

Simple LED

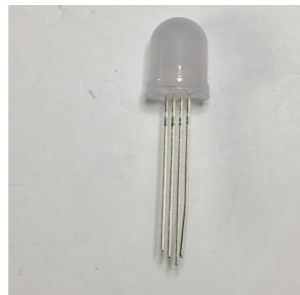

RGB LED

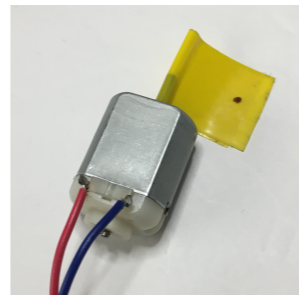

Simple Motor



Gear Motor



Solenoid

SINK (mA)