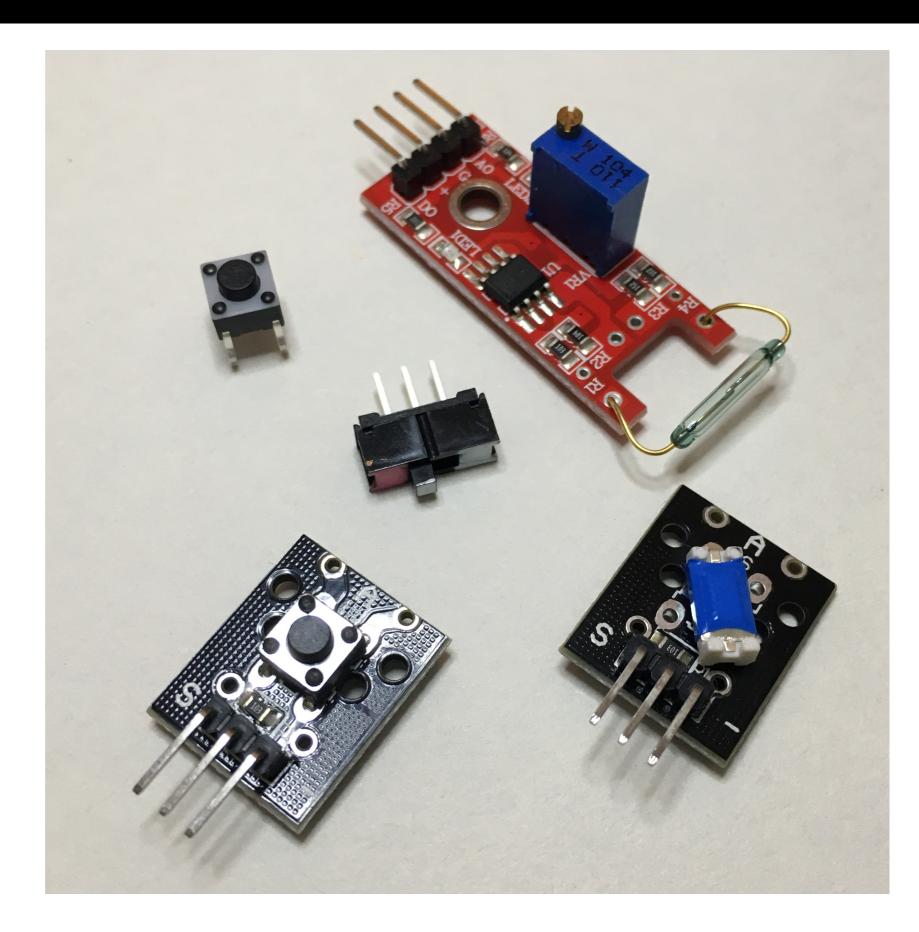
Out kits are equipped with several switches




Why are switches important?


Switches give us the ability to create inputs, and control digital signals.

They are easily overlooked but have many roles.


New Part :: Switches

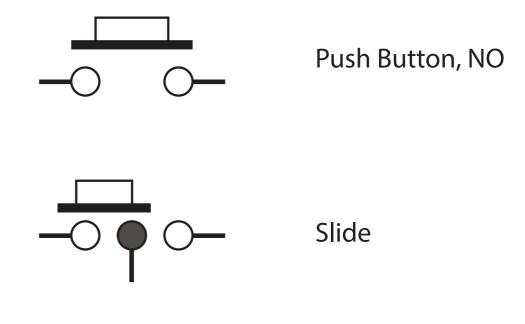
- Switches come in many flavours
- They have ∨ and I limits
- Ours are for signals, not power (on/off)




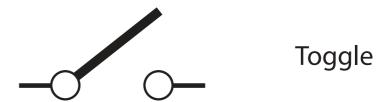



Push Button

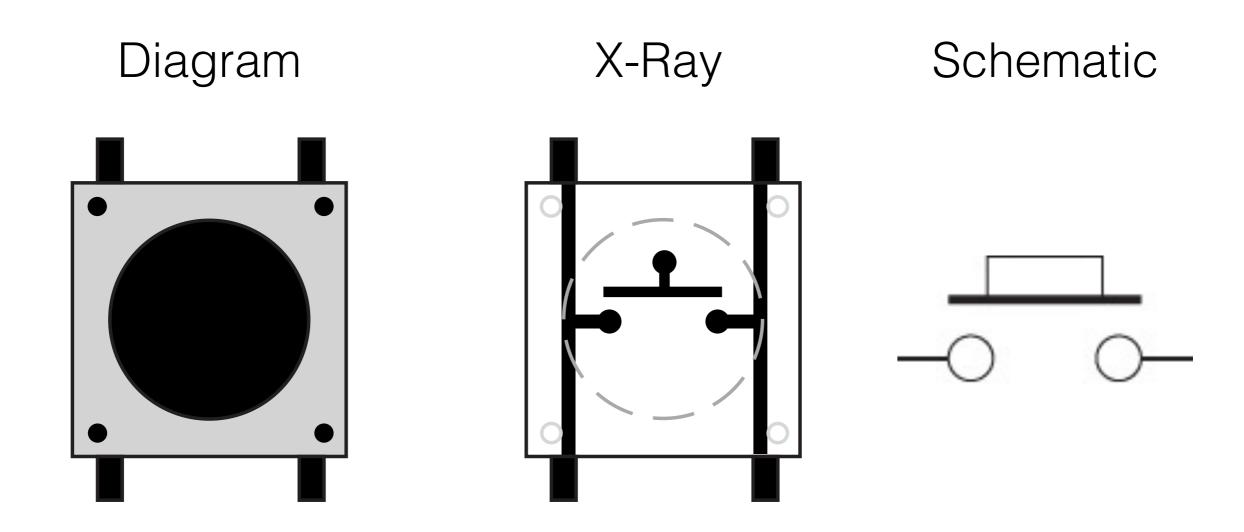

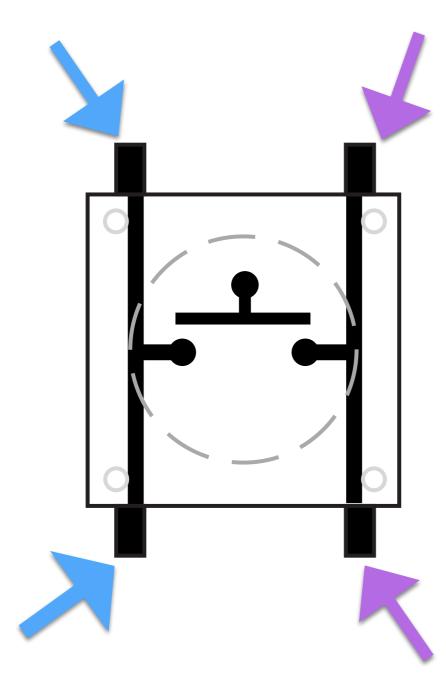

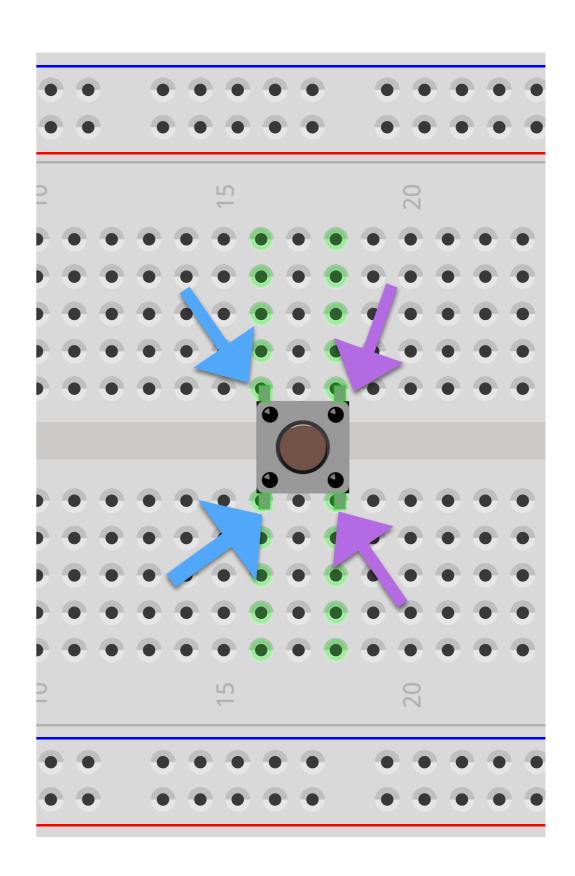

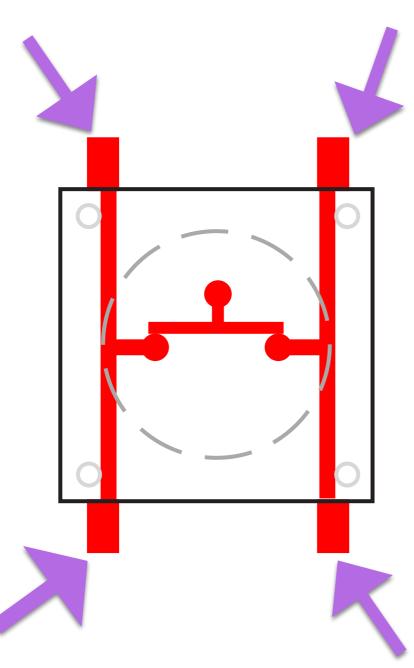

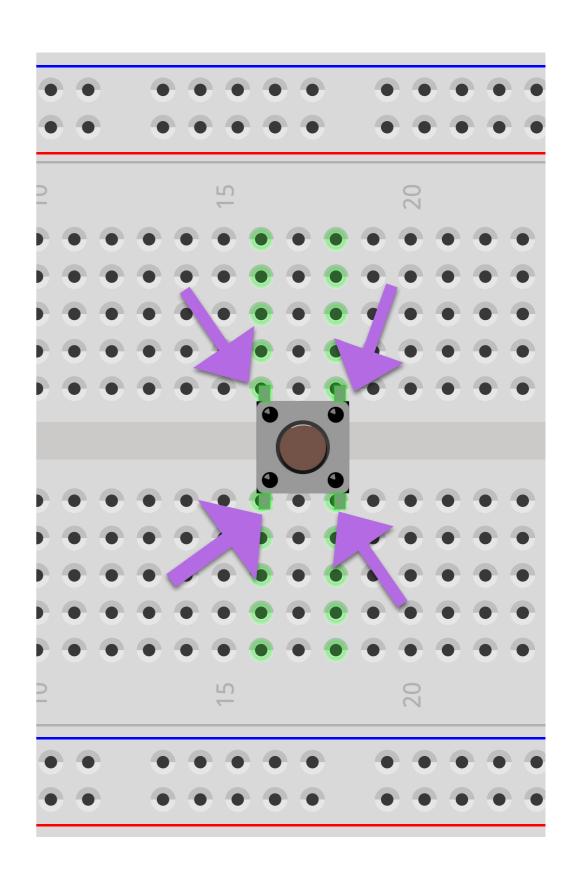

Slide

